

Enrico Nardelli

Logic Circuits and

Computer Architecture

Appendix A


Digital Logic Circuits

Part 1: Combinational Circuits

and Minimization

Structured organization

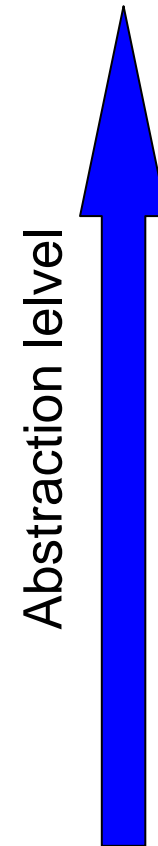- Problem-oriented language level
- Assembly language level
- Operating system machine level
- Instruction set architecture level
- Microarchitecture level
- Digital logic level




Digital Logic level

- Digital circuits
 - Only two logical levels present (i.e., binary)
 - low/high voltage
- Basic gates
 - AND, OR, NOT
- Basic circuits
 - Combinational (without memory, stateless)
 - Sequential (with memory, state dependent behaviour)

Boolean Algebra

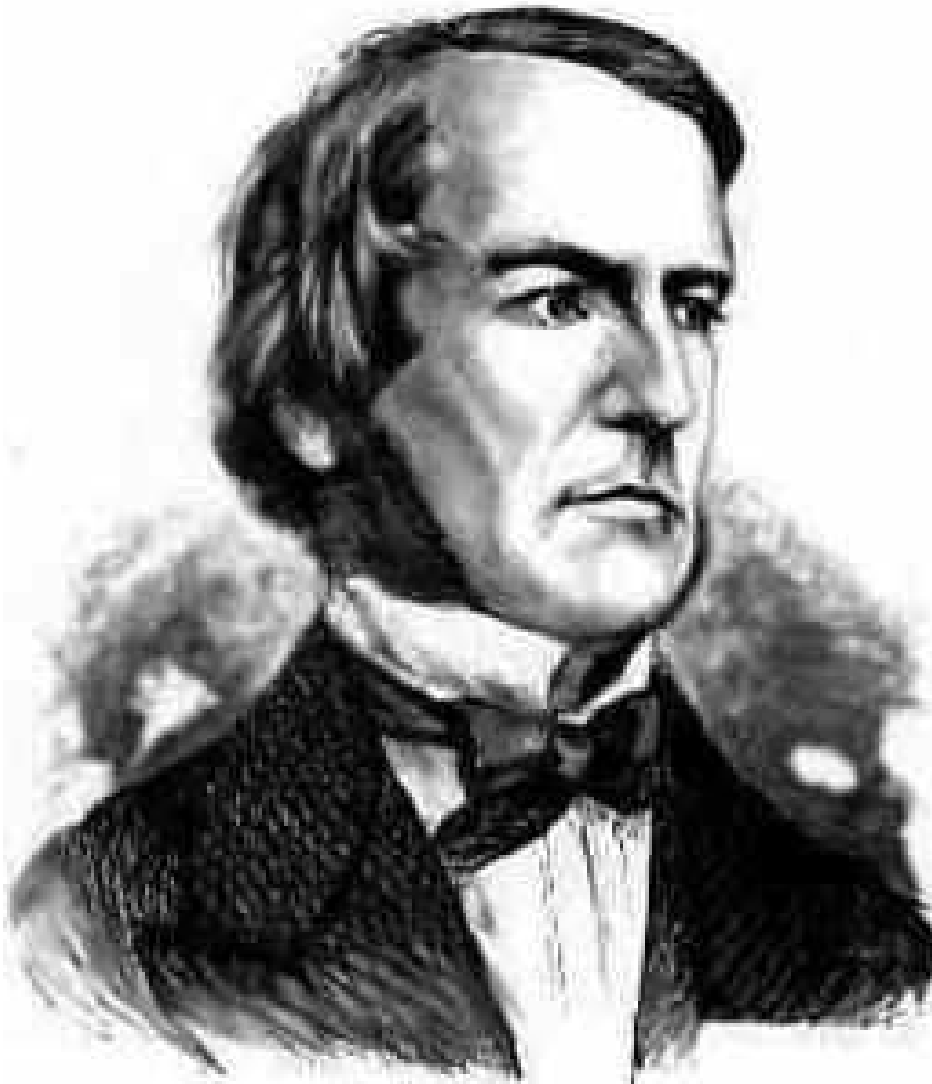- Variables: A, B, ...
- Domain of variables: 2 values
 - 1 or 0; Y or N; true or false; ...
- Fundamental Operations
 - AND, OR, NOT
- Intended meaning (for humans - *Laws of Thought*)
 - AND: both inputs are true
 - OR: at least one input is true
 - NOT: negate the input
- Named from George Boole



George Boole (1815-1864)

*An Investigation of the Laws
of Thought, on Which are
founded the Mathematical
Theories of Logic and
Probabilities (1854)*

Formal definition of functions (1)

- By means of “truth tables”
 - Explicit representation of the output for all possible inputs

A	B	AND
0	0	0
0	1	0
1	0	0
1	1	1

A	B	OR
0	0	0
0	1	1
1	0	1
1	1	1

A	NOT
0	1
1	0

Boolean functions

- Conventions

- NOT (negation): $\text{NOT}(A) = A' = \bar{A}$
- AND (conjunction): $\text{AND}(A,B) = AB = A.B$
- OR (disjunction): $\text{OR}(A,B) = A+B$

- $\text{NAND}(A,B) = \text{NOT}(\text{AND}(A,B)) = (AB)'$
- $\text{NOR}(A,B) = \text{NOT}(\text{OR}(A,B)) = (A+B)'$

Formal definition of functions (2)


- By means of “boolean equation”
- Functional description of result

$$M = \text{OR}(\text{AND}(\text{NOT}(A), \text{NOT}(B)), \text{AND}(A, B))$$

$$M = A'B' + AB$$

NOT gate - the simplest one

- NOT gate - inverts the signal

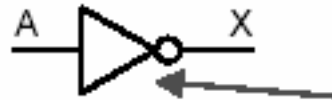


If A is 0, X is 1

If A is 1, X is 0

- A NOT gate is also called an **inverter**


AND gate

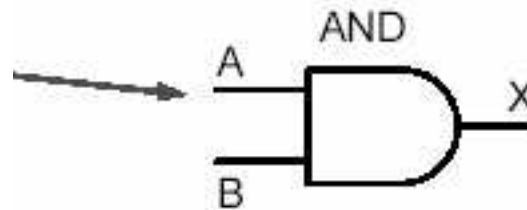- Output is 1 if all inputs are 1
 - In general, if the AND gate has N inputs, both input 1 AND input 2 AND ... AND input N must be 1 for the output to be 1
- 2-input AND gate



OR gate

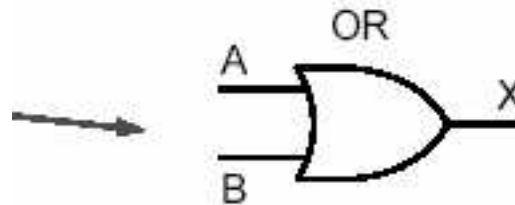- Output is 1 if at least one input is 1
 - In general, if the OR gate has N inputs, input 1 OR input 2 OR ... OR input N must be 1 for the output to be 1
- 2-input OR gate



A more complex example

- 2-input “equivalence” circuit
- The output is 1 if the inputs are the same
 - (i.e., both 0 or both 1)

- Boolean function:

$$M = A'B' + AB$$


Truth table

A	B	M
0	0	1
0	1	0
1	0	0
1	1	1


Formal definition of functions (3)

- By means of **logic circuits**
 - Combination of logic gates joined by wires

A	B	M
0	0	1
0	1	0
1	0	0
1	1	1

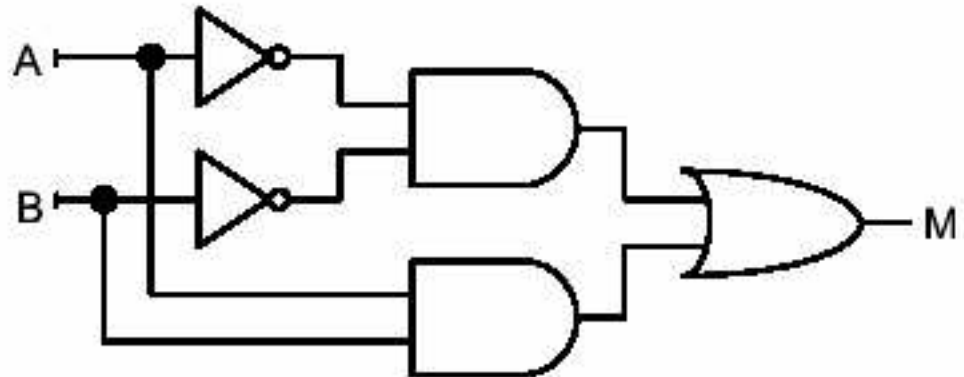

Conventions for logic circuits

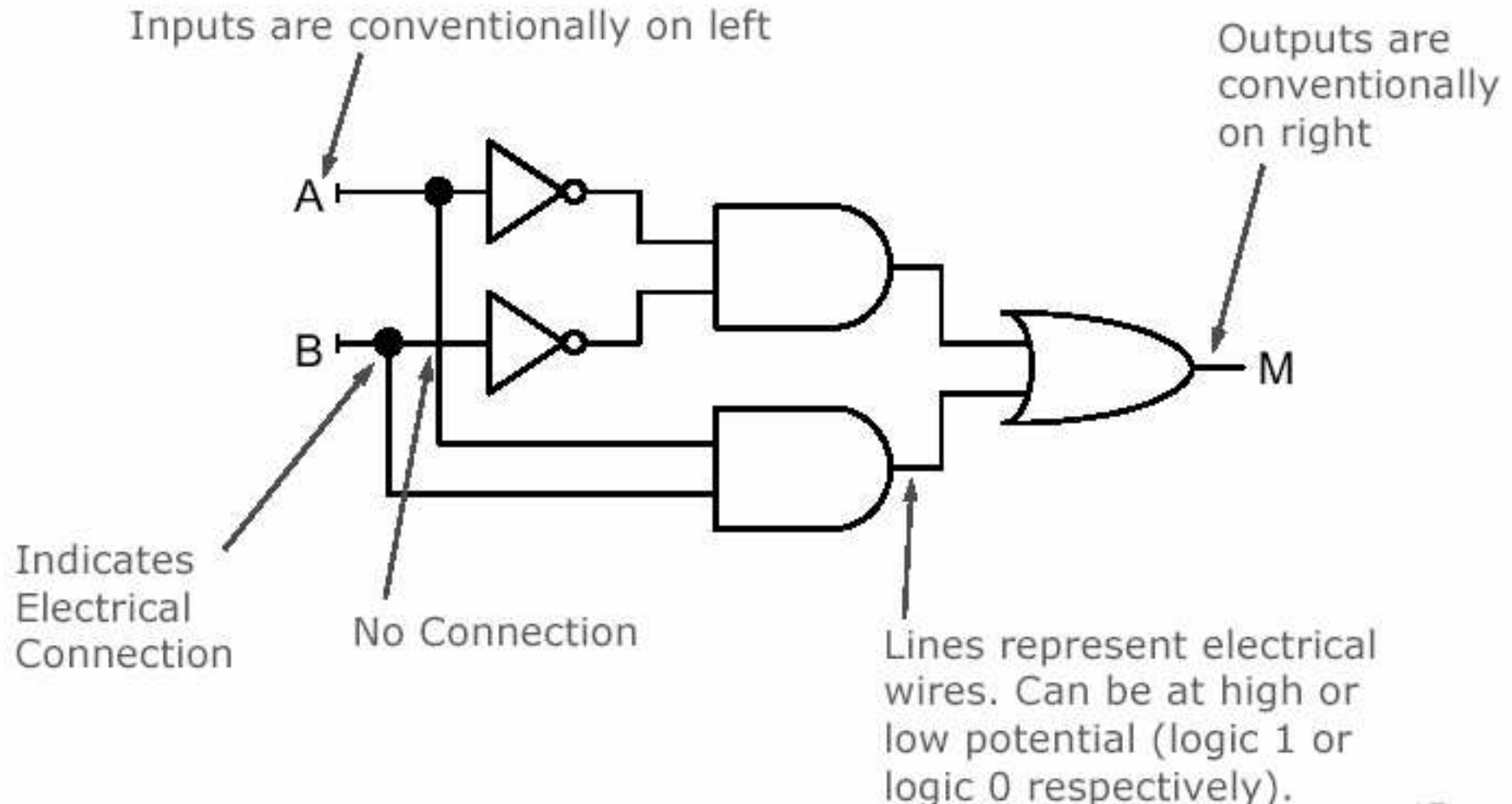

Exercise (1)


- Write the truth table and the logic circuit for

$$F = X + Y'Z$$

Truth table


X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Logic Circuit

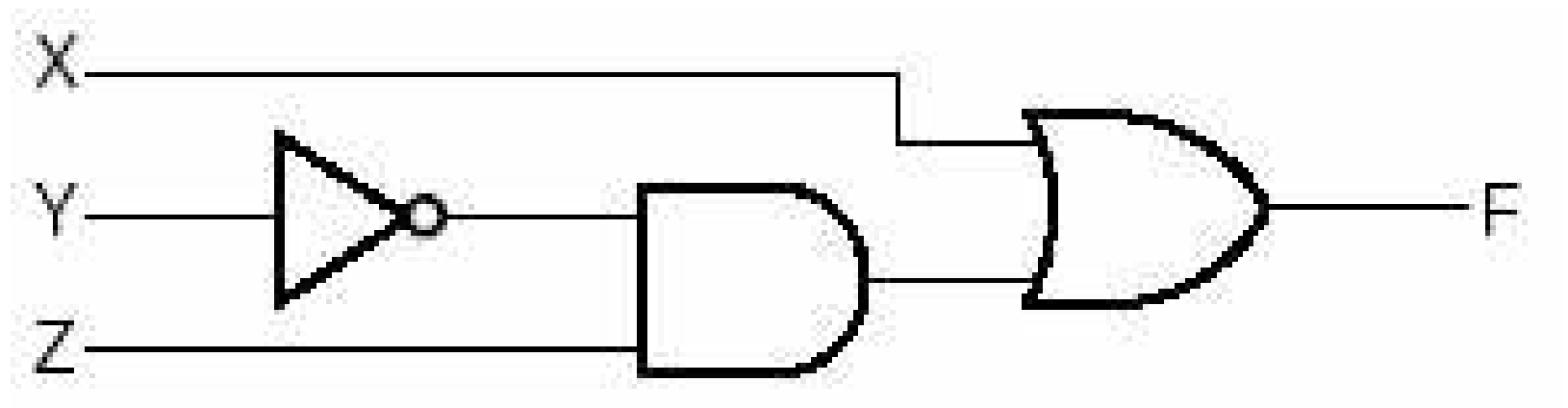

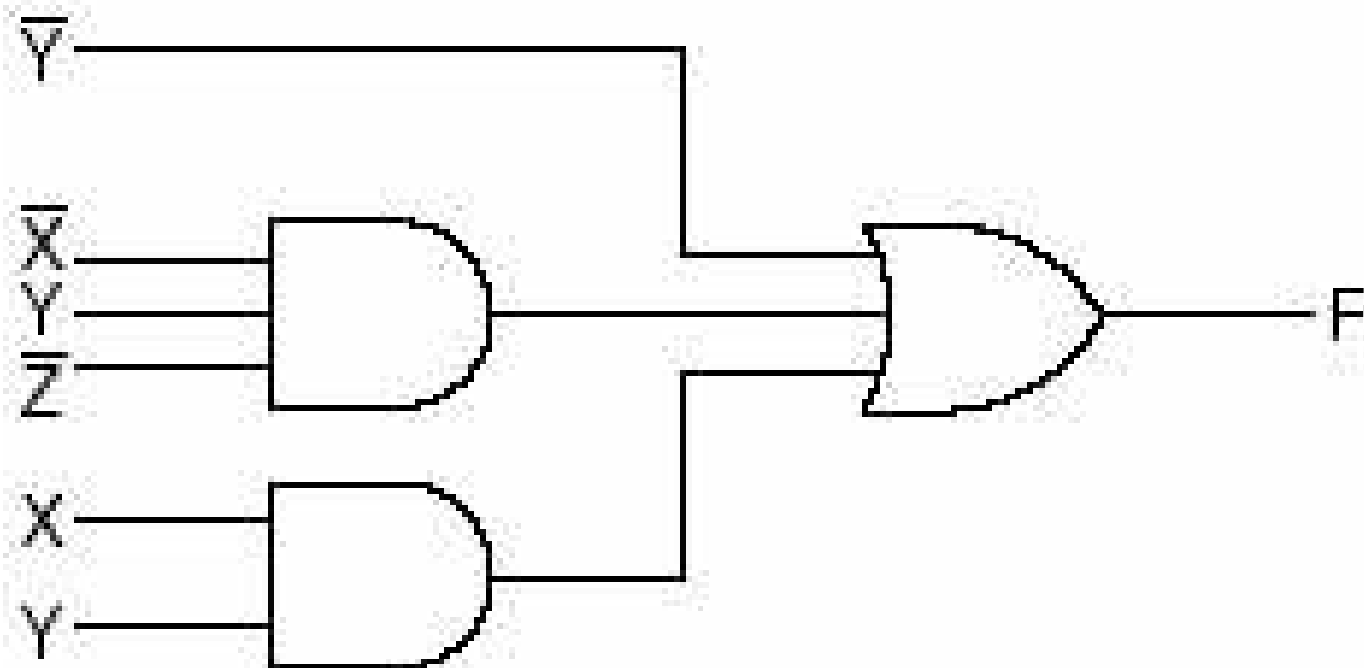Exercise (2)

- Write the boolean function and its truth table for the following logic circuit




Function and Truth Table

- $F = Y' + X'YZ' + XY$

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

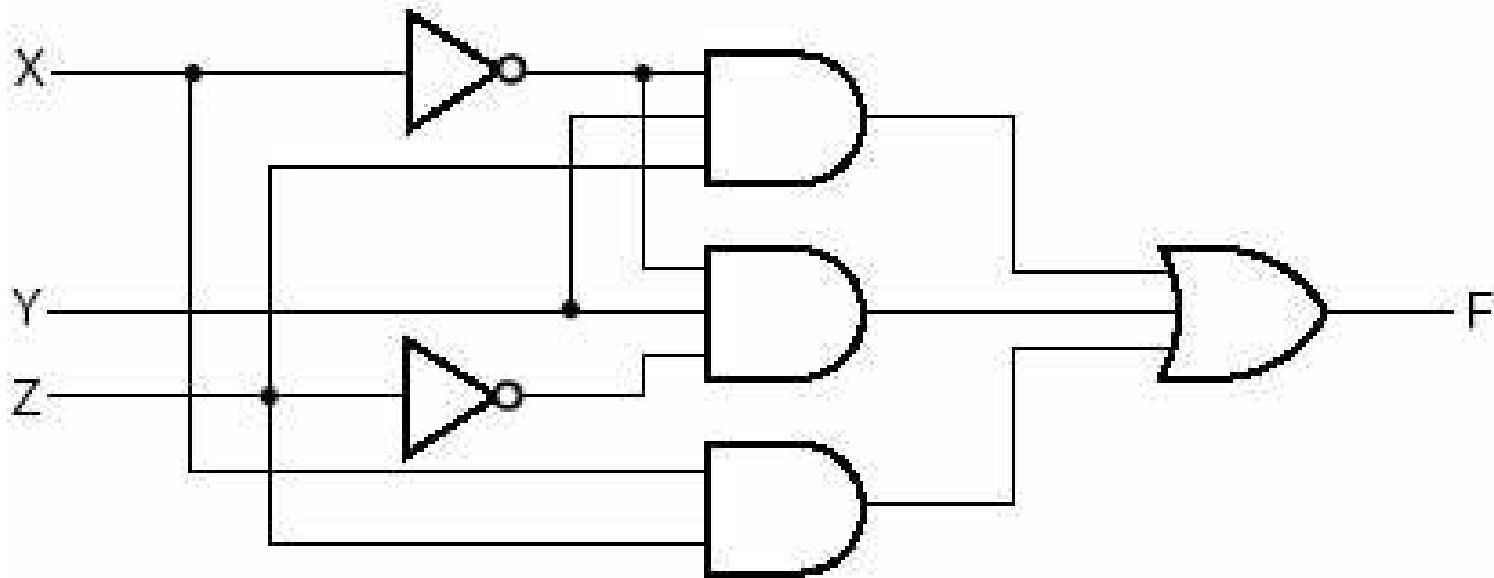Exercise (3)

- Write the boolean function and its truth table for the following logic circuit




Function and Truth Table

- $F = X'YZ + X'YZ' + XZ$

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

A simpler equivalent circuit

- $F = X'Y + XZ$

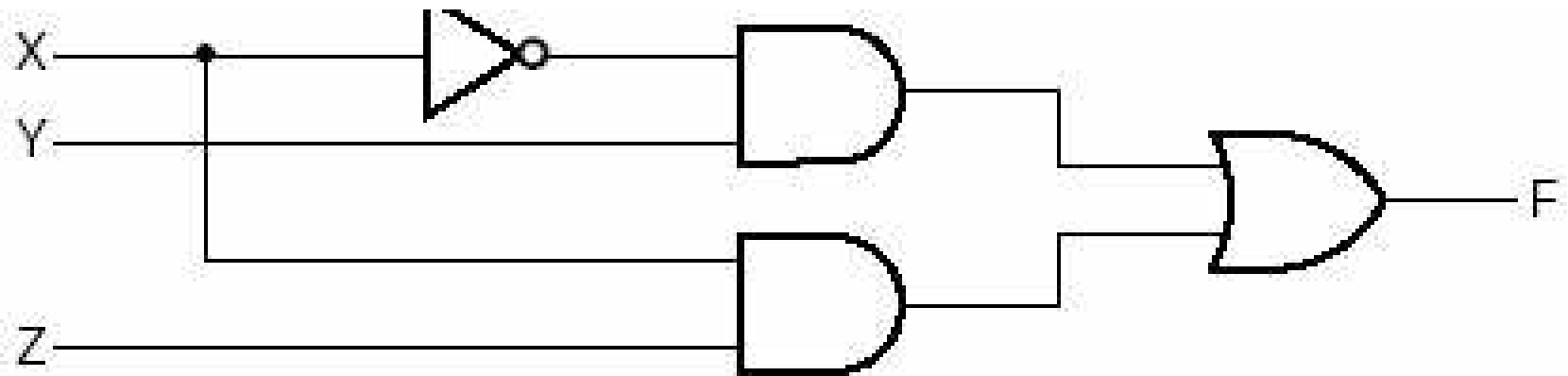

Conversion between represent.

- Circuit ->
 - > Boolean formula (left-to-right inspection)
 - > Truth table (explicit case-by-case computation)
- Boolean formula ->
 - > Circuit (to “normal” form, then inspection)
 - > Truth table (explicit case-by-case computation)
- Truth table ->
 - > Circuit (through boolean formula)
 - > Boolean formula (explicit case-by-case)

Boolean Identities

$$1A = A$$

$$0A = 0$$

$$AA = A$$

$$AA' = 0$$

$$AB = BA$$

$$(AB)C = A(BC)$$

$$A+BC = (A+B)(A+C)$$

$$A(A+B) = A$$

$$(AB)' = A' + B'$$

$$0+A = A$$

$$1+A = 1$$

$$A+A = A$$

$$A+A' = 1$$

$$A+B = B+A$$

$$(A+B)+C = A+(B+C)$$

$$A(B+C) = AB+AC$$

$$A+AB = A$$

$$(A+B)' = A'B'$$

Identity

Null

Idempotent

Inverse

Commutative

Associative

Distributive

Absorption





De Morgan

Truth tables to verify De Morgan's theorem

A)	X	Y	$X + Y$	$\overline{X + Y}$	B)	X	Y	\bar{X}	\bar{Y}	$\bar{X} \cdot \bar{Y}$
	0	0	0	1		0	0	1	1	1
	0	1	1	0		0	1	1	0	0
	1	0	1	0		1	0	0	1	0
	1	1	1	0		1	1	0	0	0

De Morgan circuit equivalents

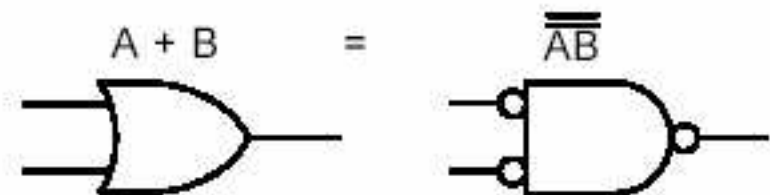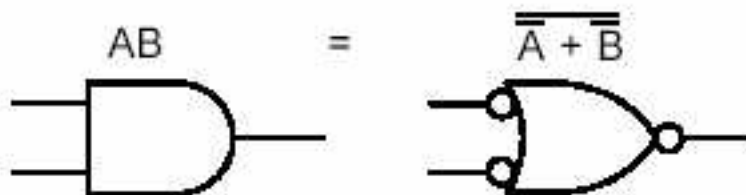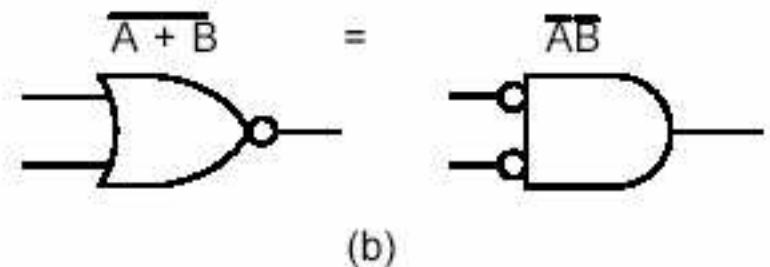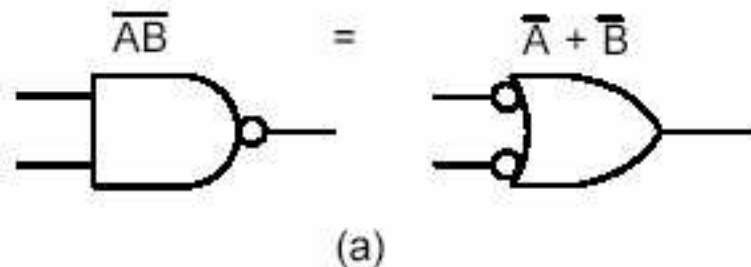- AND/OR can be interchanged if you invert the inputs and outputs




NAND gate - the negation of AND

- The opposite of the AND gate is the NAND gate (output is 0 if all inputs are 1)

Truth table

- Logic diagram

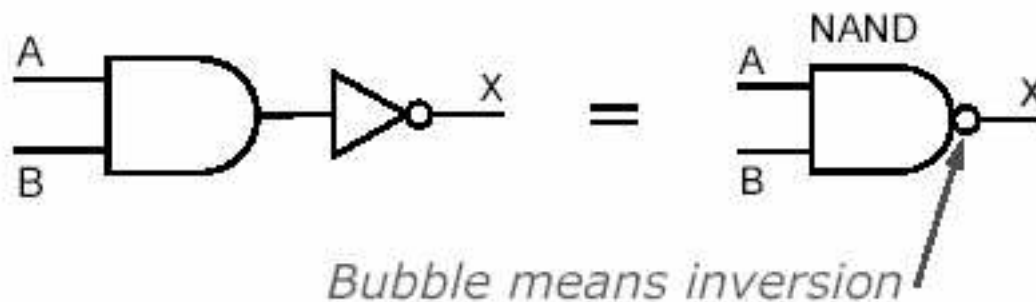


A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

NOR gate - the negation of OR

- The opposite of the OR gate is the NOR gate (output is 0 if any input is 1)

- Logic diagram

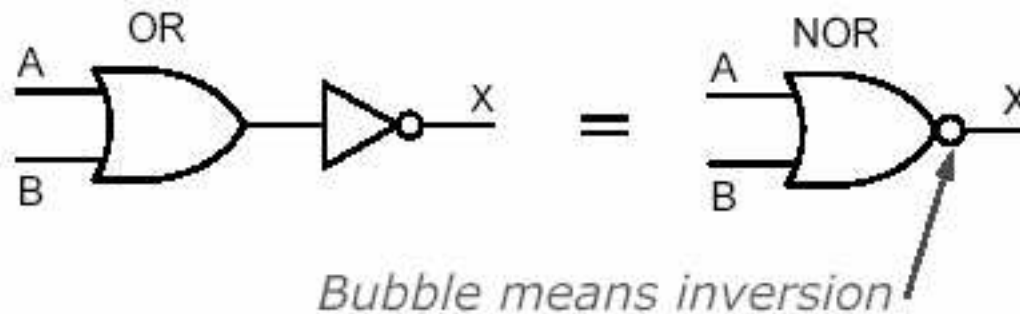

Truth table

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

Exercise


- Write the truth table for:
 - a 3 input NAND gate
 - a 3 input NOR gate

XOR gate - the exclusive OR

- For a 2-input gate
 - Output is 1 if exactly one of the inputs is 1

Truth table

- Logic diagram

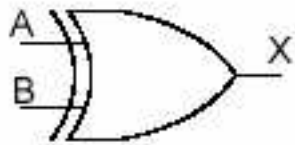

- For > 2 inputs: output is 1 if an odd number of inputs is 1

A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Universal Gates

- How many logical functions there are?
- With n inputs there are $2^{(2^n)}$ possible logical functions

A	B	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1


Universal Gates (2)

- AND, OR, NOT can generate all possible boolean functions (**boolean algebra**)
- Is it possible to use fewer basic operations?

Universal Gates (3)



- AND, NOT are enough !
- OR, NOT are enough !
- Even NAND alone or NOR alone are enough !

How NAND simulates AND, OR


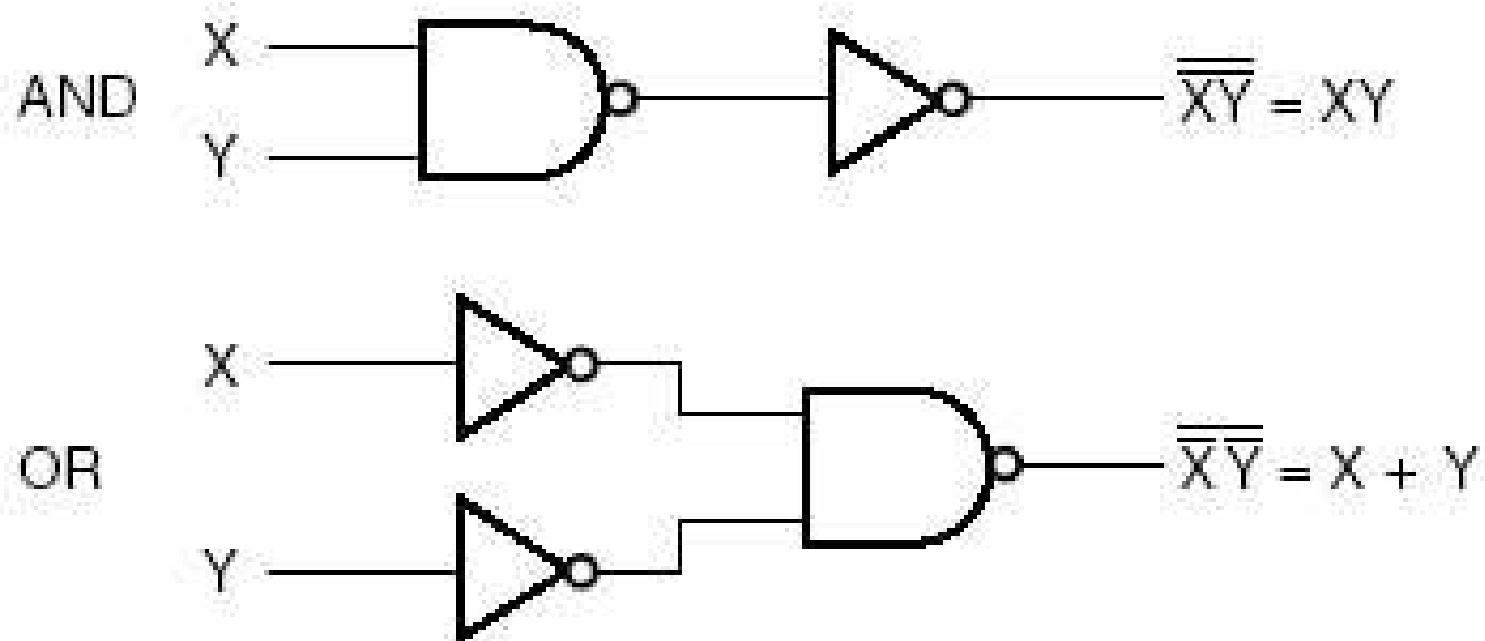


- Simulation of NOT ???

Alternative NAND representations

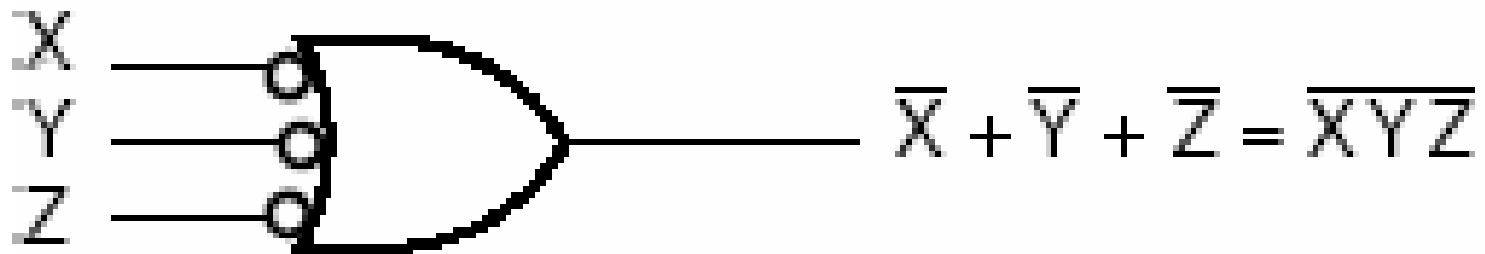
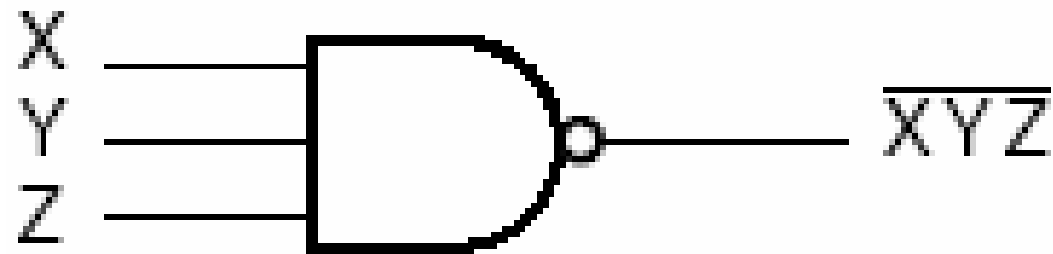


How NOR simulates AND, OR

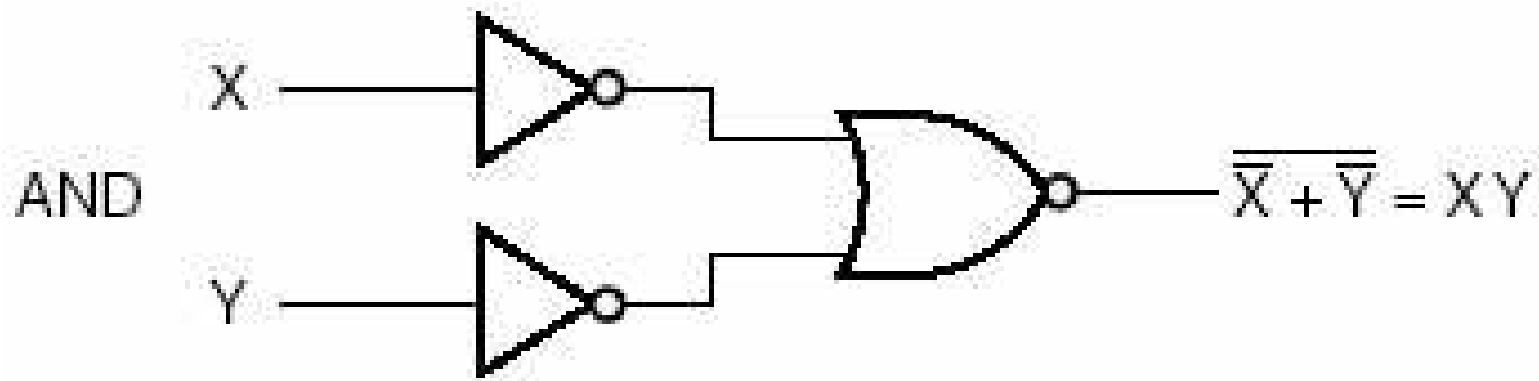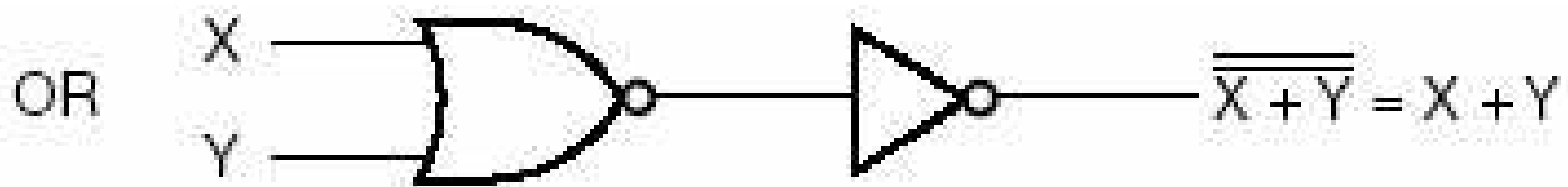


- Simulation of NOT ???

Alternative NOR representations

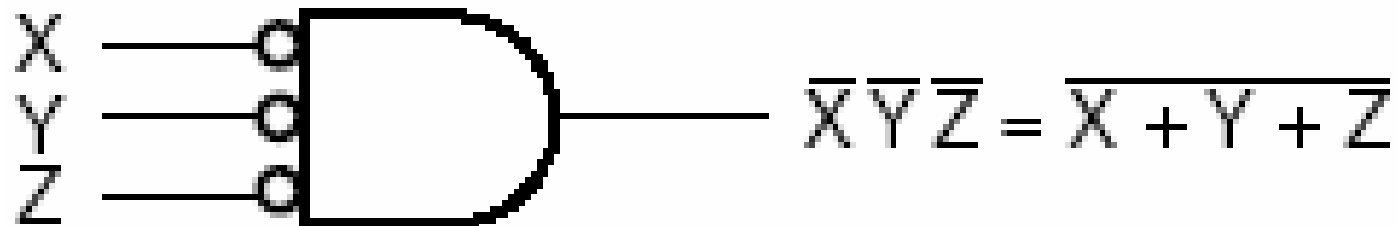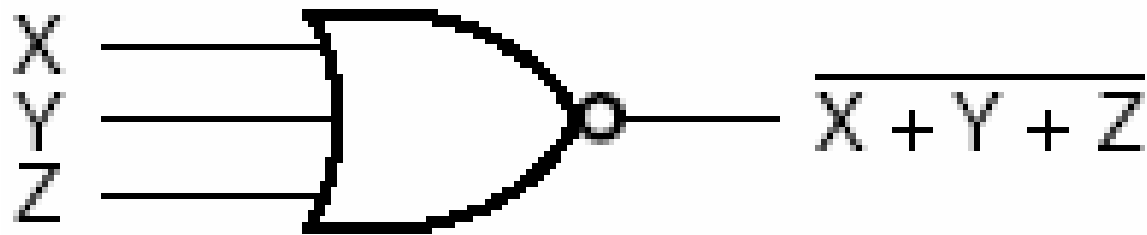

Gate equivalence

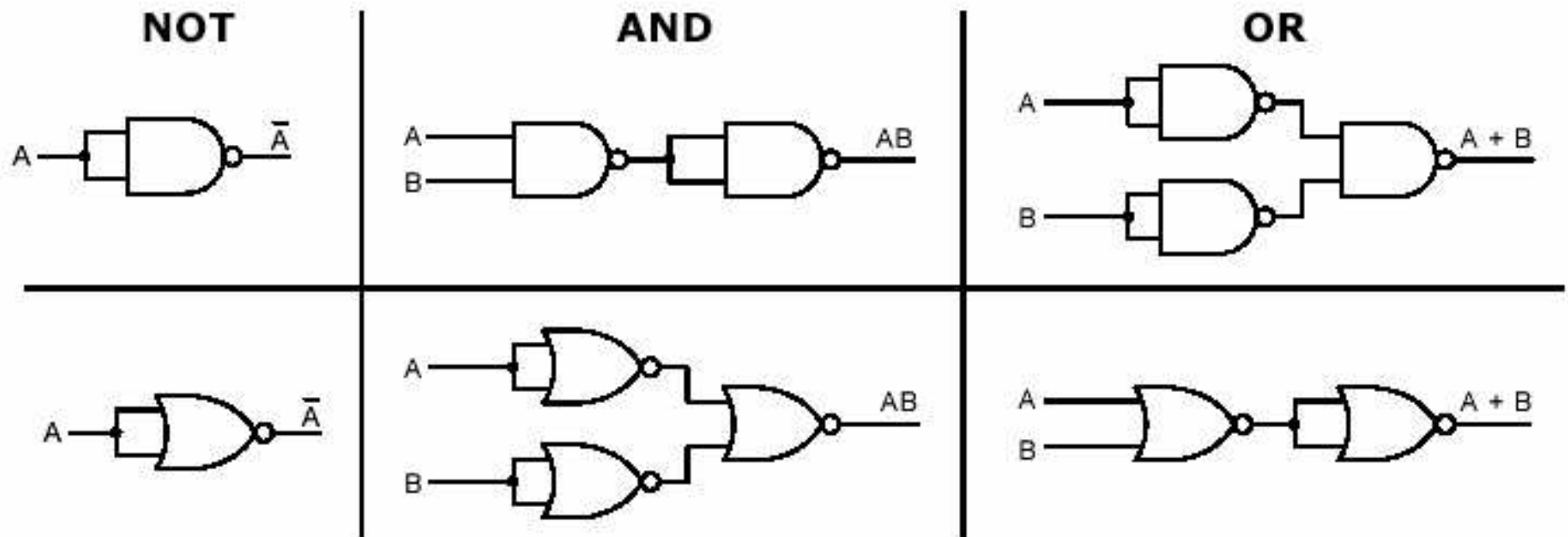
- Any AND, OR, NOT gate can be obtained using just NAND gates or just NOR gates



- Consequence: any circuit can be constructed using just NAND gates or just NOR gates (easier to build)


Equivalence modifications (1)

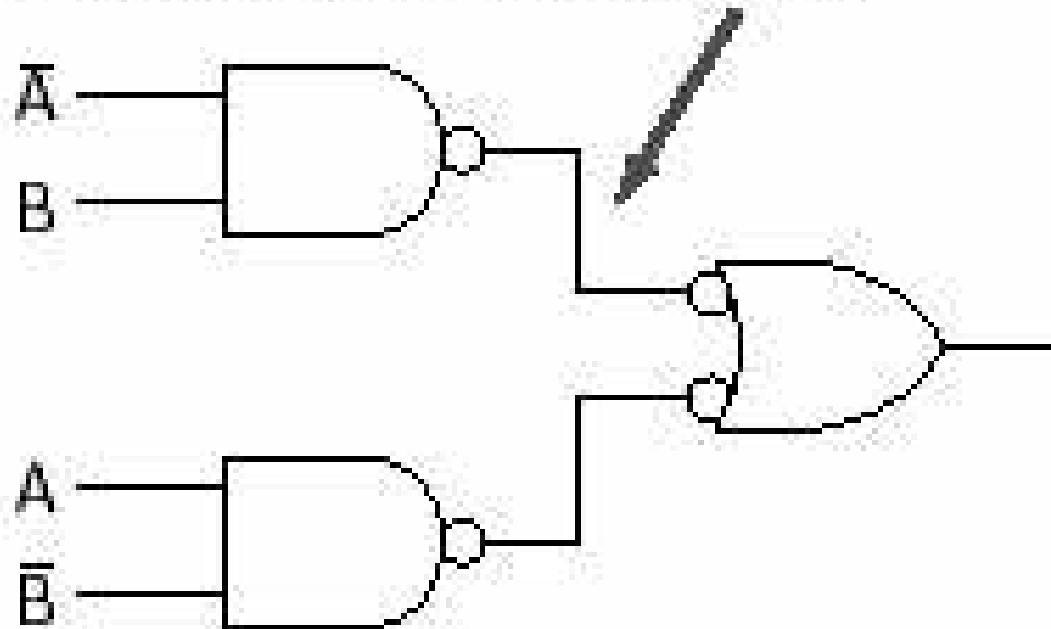On any wire, you can introduce a bubble at beginning and end




Equivalence modifications (2)

- Substitute equivalent gates

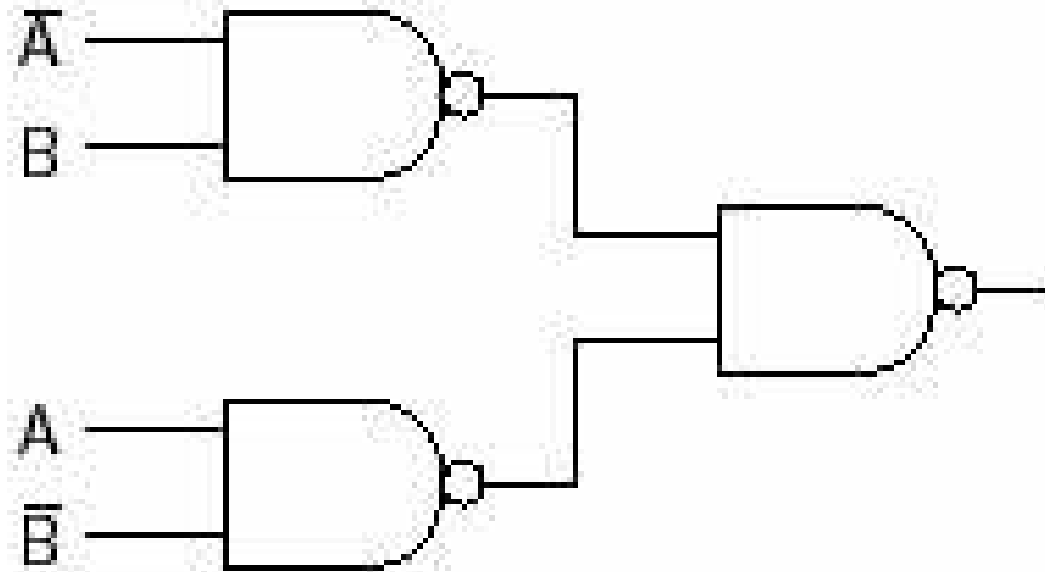


Transforming OR, AND to NAND

- Transform the following circuit

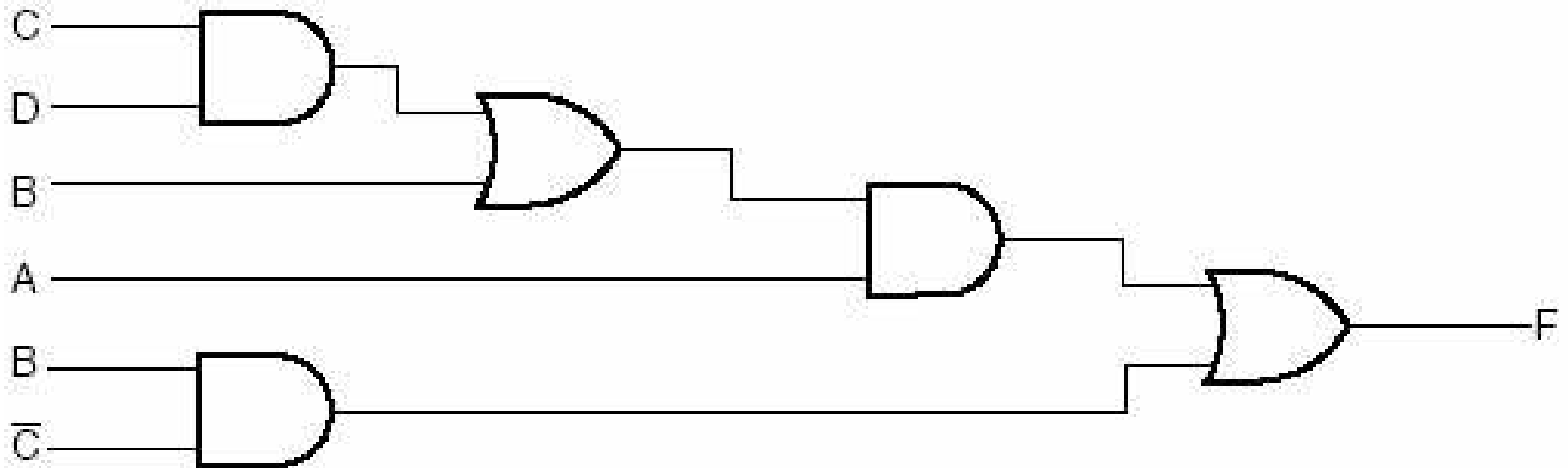

Solution


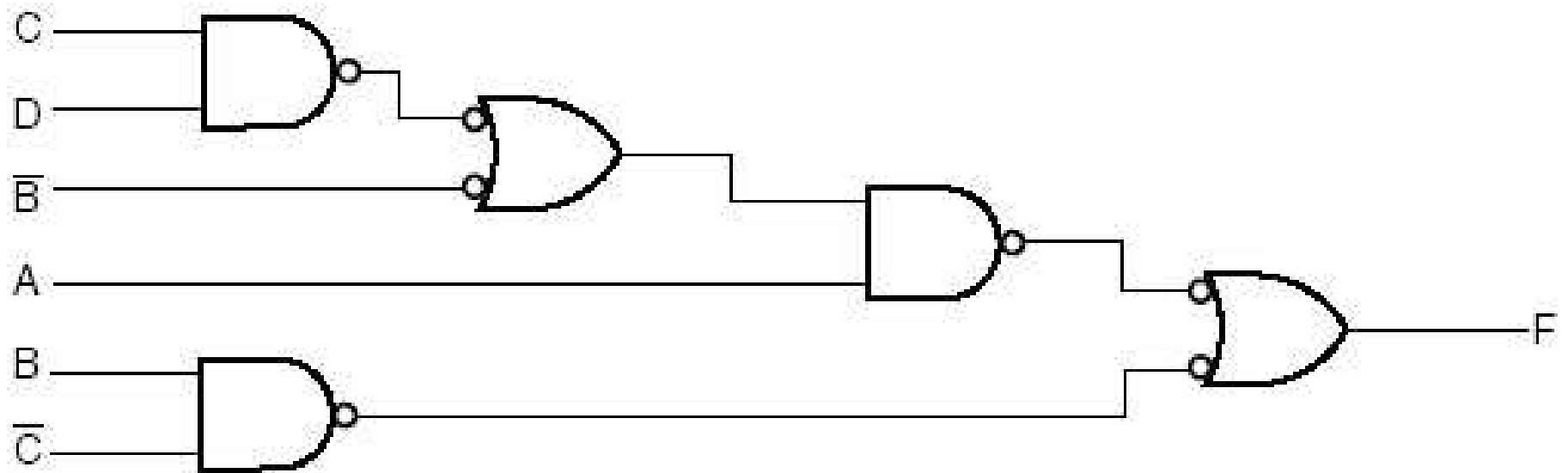


Exercise

- Write a NAND only logic circuit for

$$F = XY' + X'Y + Z$$

Solution

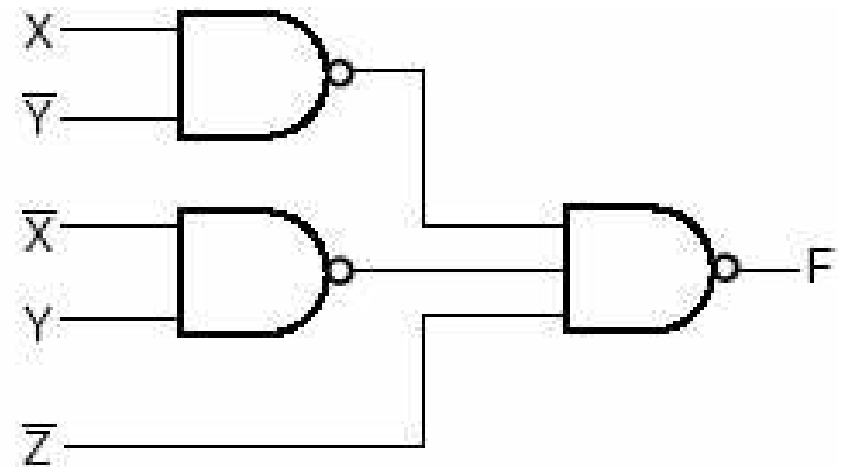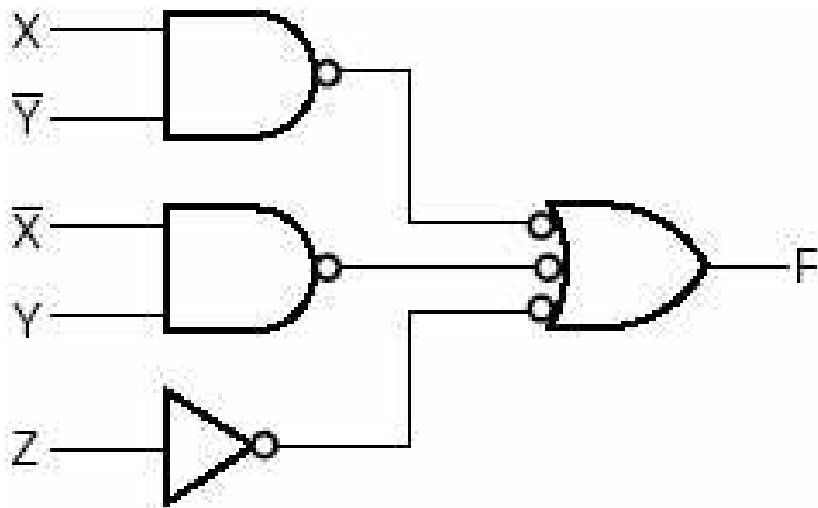

Exercise

- Write a NAND only logic circuit for the exclusive OR function (XOR)


$$\text{XOR}(A,B) = A'B + AB'$$

Solution (1)


- Truth table

A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0


initial circuit

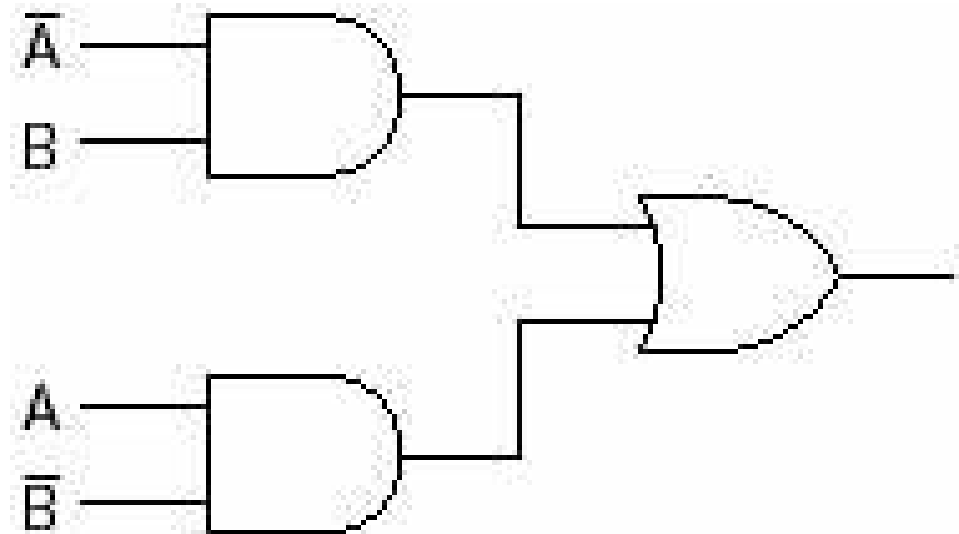


Solution (2): equivalence transform.

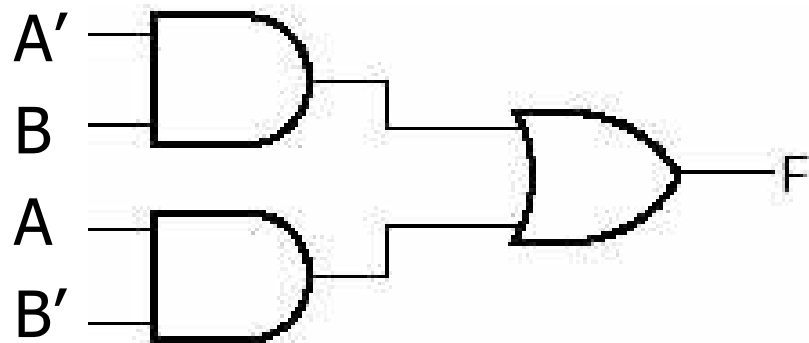

(a)

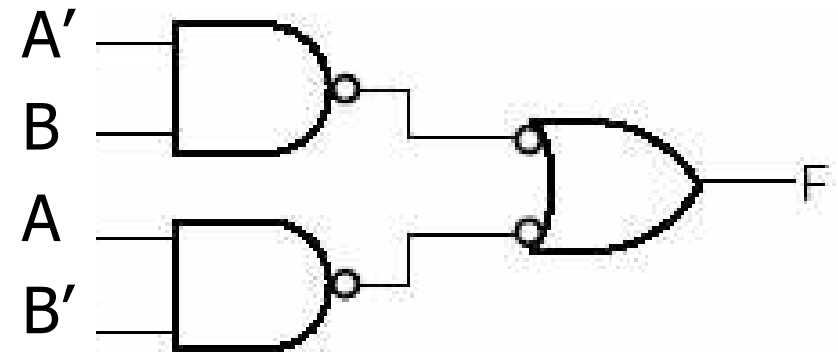

(b)

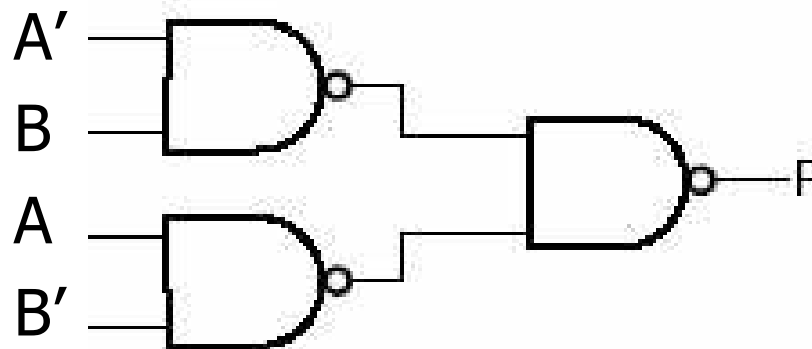


Exercise

- Write a NOR only logic circuit for

$$F = (A+D)(C+D)E$$

Solution

- Direct realization

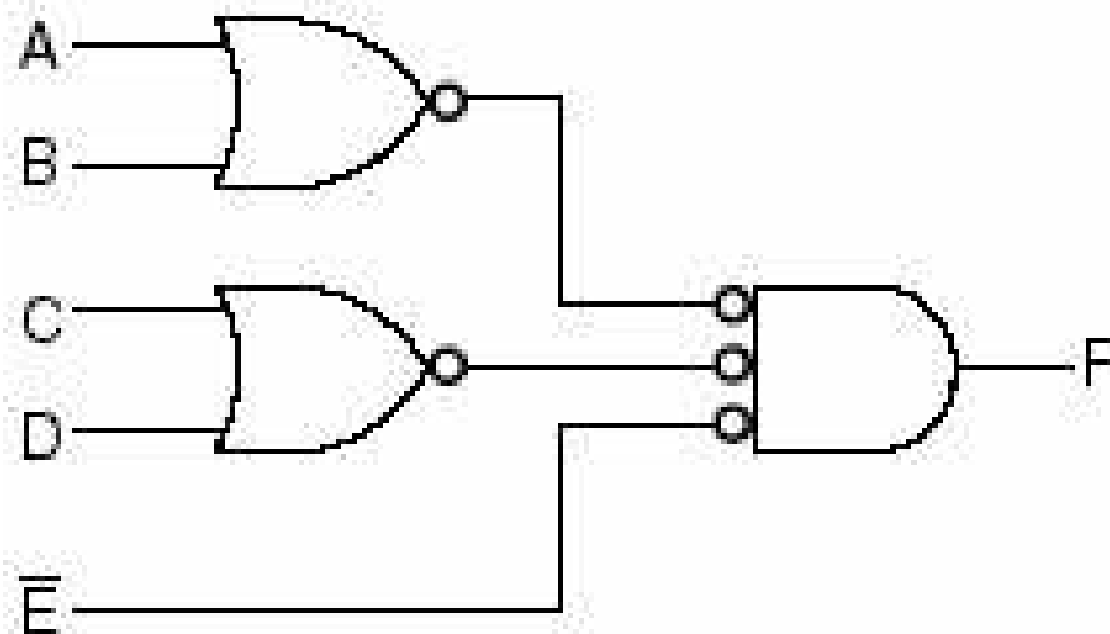


Boolean function implementation

- Any function can be implemented as the OR of the AND combinations of its inputs
 - Called **sum of products** (SOP)
- Start from the truth table
 - For each 1 in the output
 - Write its inputs in AND
 - Write these in OR
- $M = A'BC + AB'C + ABC' + ABC$


A	B	C	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Equivalent Logic Circuit

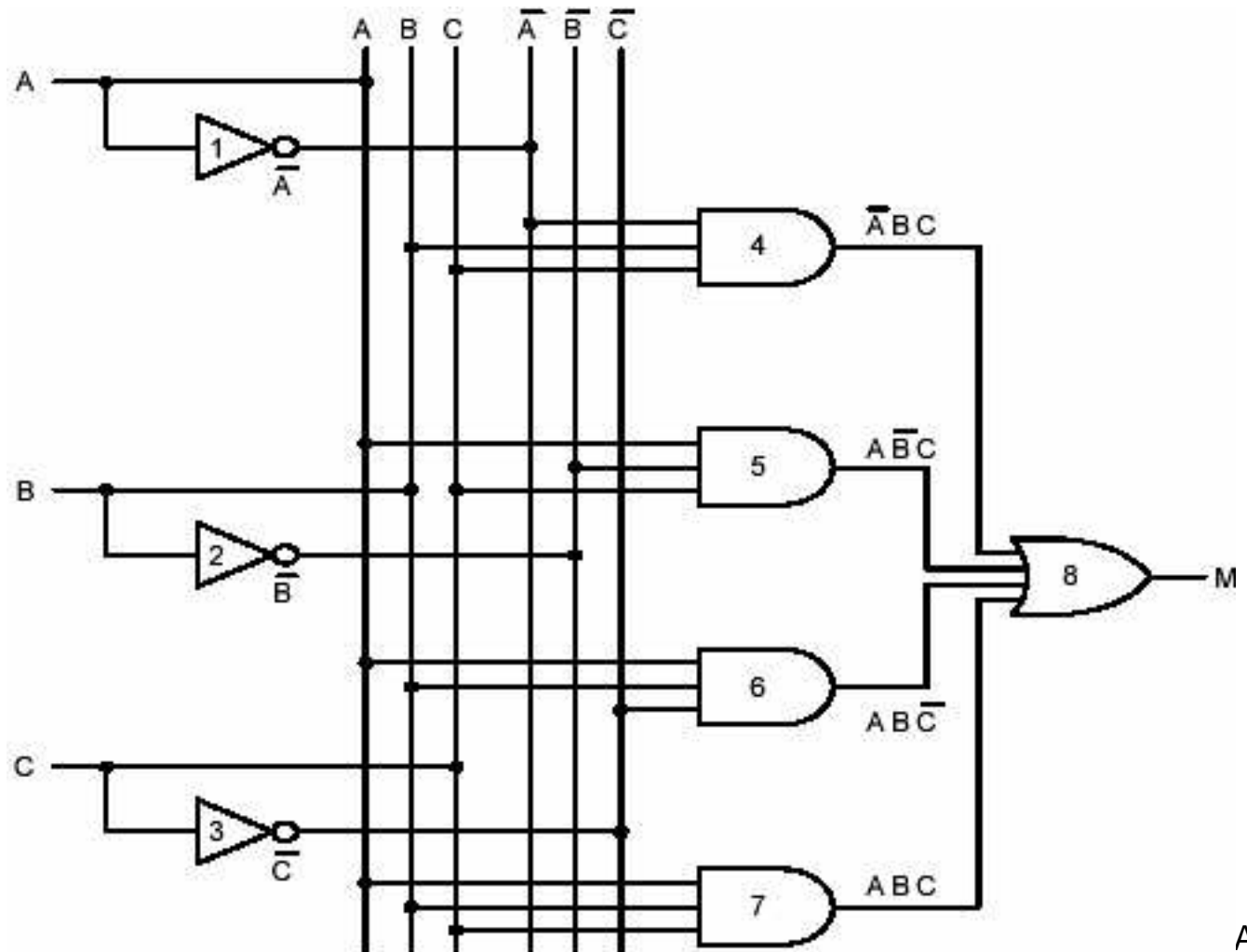

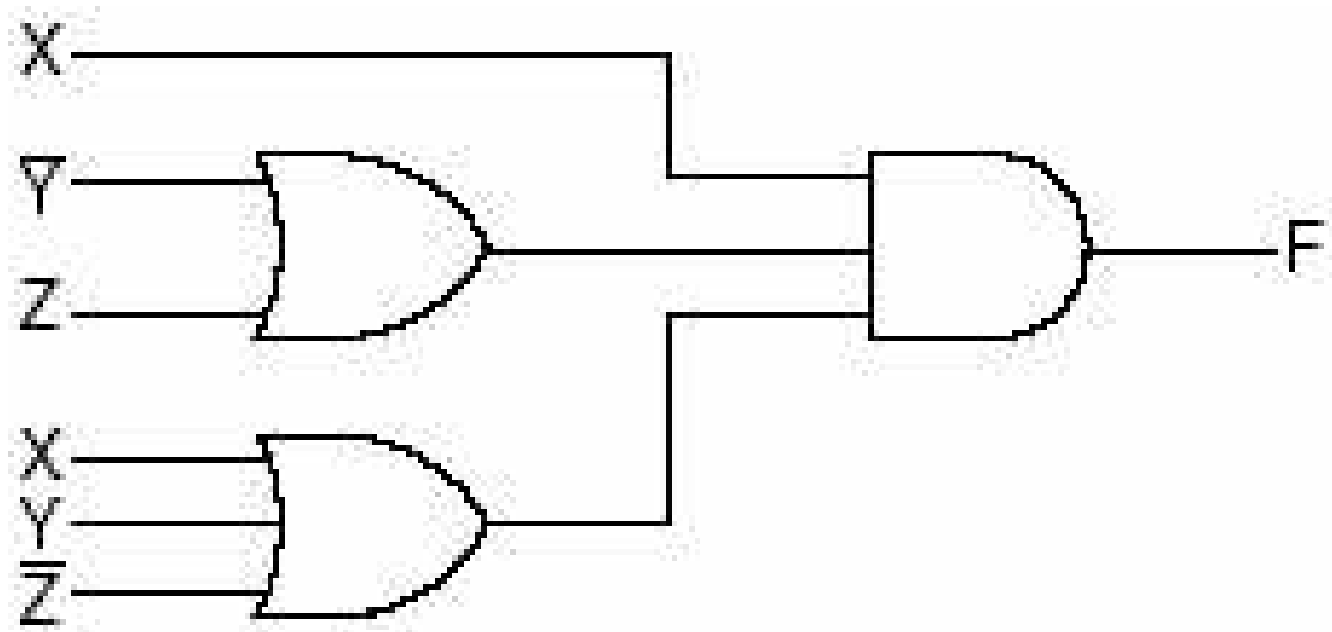Exercise


- Write the boolean function and its truth table for the following logic circuit



Solution: truth table

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Solution: boolean formula
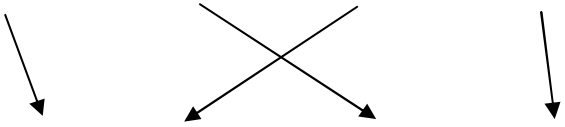
$$\begin{aligned} F &= X.(Y'+Z).(X+Y+Z') \\ &= (XY'+XZ).(X+Y+Z') \\ &= XY'X + XY'Y + XY'Z' + XZX + XZY + XZZ' \\ &= XY' + XY'Z' + XZ + XZY \\ &= X(Y'+Z) + X(Y'Z' + YZ) \end{aligned}$$


N.B.: $Y'Z' + YZ$ is not 1 !!!

Exercise

- Express $Z = (A(B + C(A' + B')))'$ as sum of products

Solution

$$\begin{aligned} Z &= (A(B+C(A'+B')))' \\ &= A' + (B+C(A'+B'))' \\ &= A' + B'(C(A'+B'))' \\ &= A' + B'(C' + (A'+B')') \\ &= A' + B'(C' + AB) \\ &= A' + B'C' + ABB' \\ &= A' + B'C' + A0 \\ &= A' + B'C' + 0 \qquad = A' + B'C' \end{aligned}$$

Boolean function implem. (2)

- Any function can be implemented as the AND of the OR combinations of its inputs
 - Called **product of sums** (POS)
- Start from the truth table
 - For each 0 in the output
 - Write its inputs in AND
 - Write these **negated** in AND
 - Obtain $F = Z_0' \cdot Z_1' \cdot Z_2' \dots$
 - Finally, apply De Morgan to F

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Boolean function implem. (3)

- De Morgan (general): $(ABC)' = A' + B' + C'$
- $$\begin{aligned} F &= (A'B'C')' \cdot (A'B'C)' \cdot (AB'C')' \cdot (AB'C)' \cdot (ABC)' \\ &= (A'' + B'' + C'') \cdot (A'' + B'' + C') \cdot (A' + B'' + C'') \cdot \\ &\quad \cdot (A' + B'' + C') \cdot (A' + B' + C') \\ &= (A + B + C) \cdot (A + B + C') \cdot (A' + B + C) \cdot \\ &\quad \cdot (A' + B + C') \cdot (A' + B' + C') \end{aligned}$$

Boolean function implem. (4)

- Shortcut procedure for POS form (use only if you know what you are doing!)
 - Complement the table by substituting everywhere a 0 with a 1 and a 1 with a 0
 - Write a SOP form for the complemented table
 - Complement the formula by substituting everywhere and AND with an OR and an OR with an AND
 - Why does it work ???


Canonical Form for boolean functions

- It is a “standard” way of expressing SOP or POS supporting realization by means of standard electronic components
- It is:
 - a sum of minterms, for SOP
 - a product of maxterms for POS
- A minterm is a product containing all variables, either in the positive form or in the negative form
- A maxterm is a sum containing all variables, either in the positive or in the negative form.
- Examples:
 $F = (A' + B + C) \cdot (B' + C)$ is **not** in a POS canonical form
 $M = AB + A'BC$ is **not** in a SOP canonical form

Standard implementation

- Given a boolean function expressed as sum of products or as product of sums it can be directly implemented in a circuit
- PLA: programmable logic array
- A PLA for sum of products is made by a first module combining inputs to form products, followed by a second module combining products to give the desired function

Schema for a sum-of-products PLA

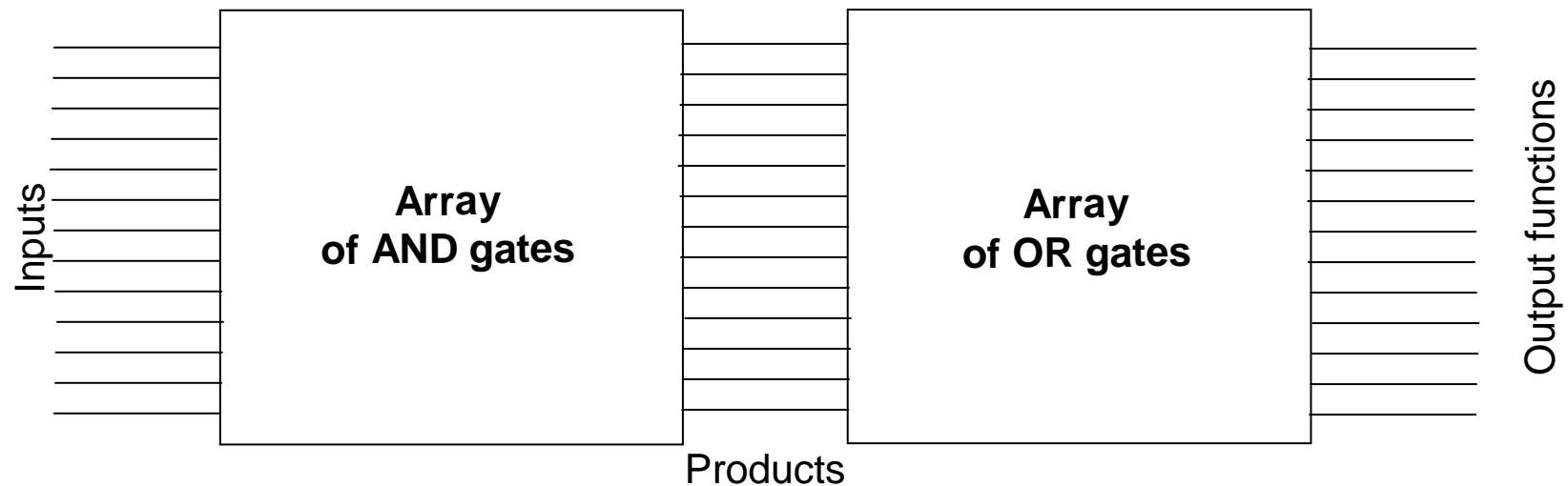


- Inputs are variables and their negation
- Each output line realizes a boolean function


An example

A	B	C	W	X	Y
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

The PLA implementation

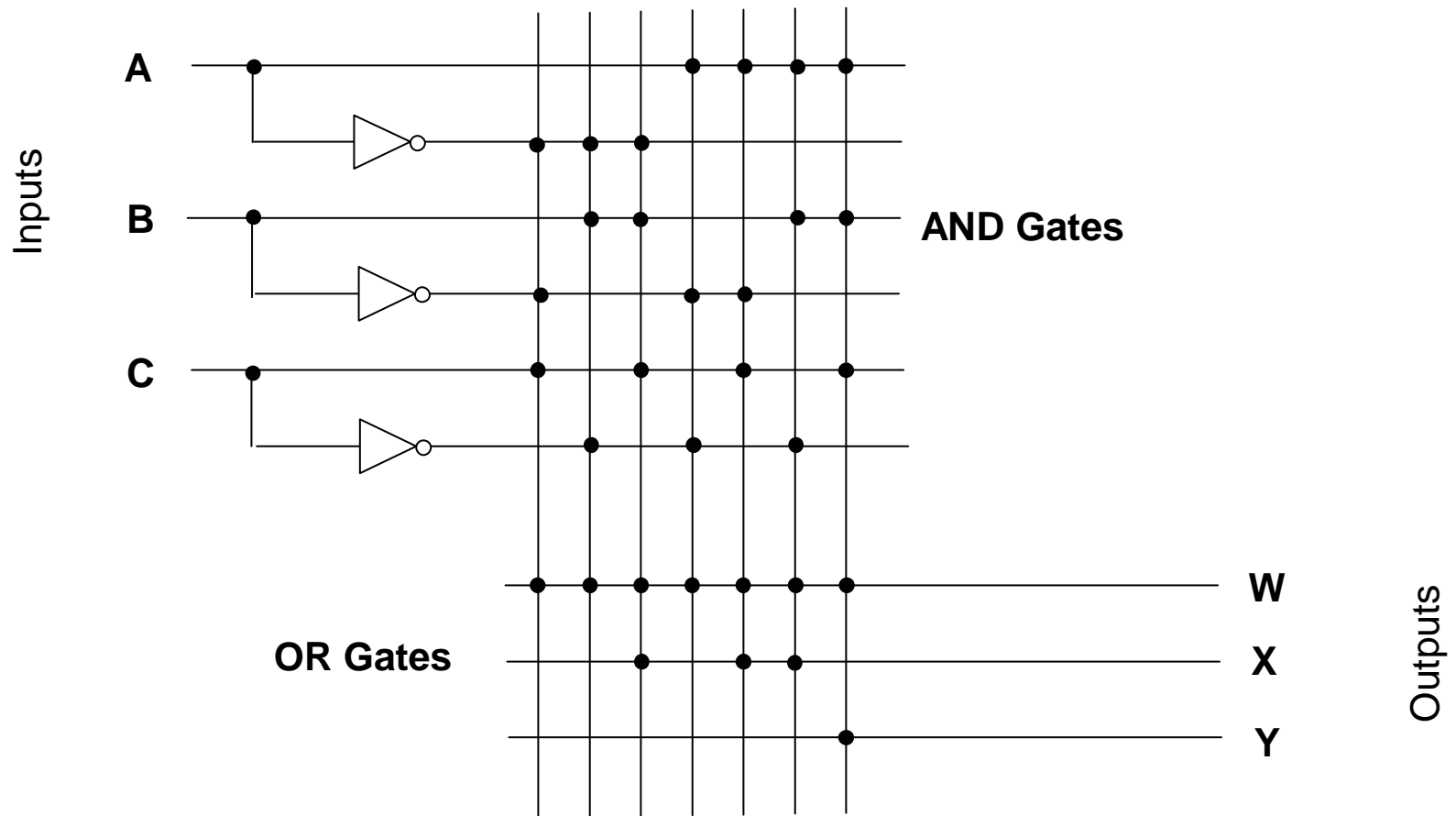

Real circuits

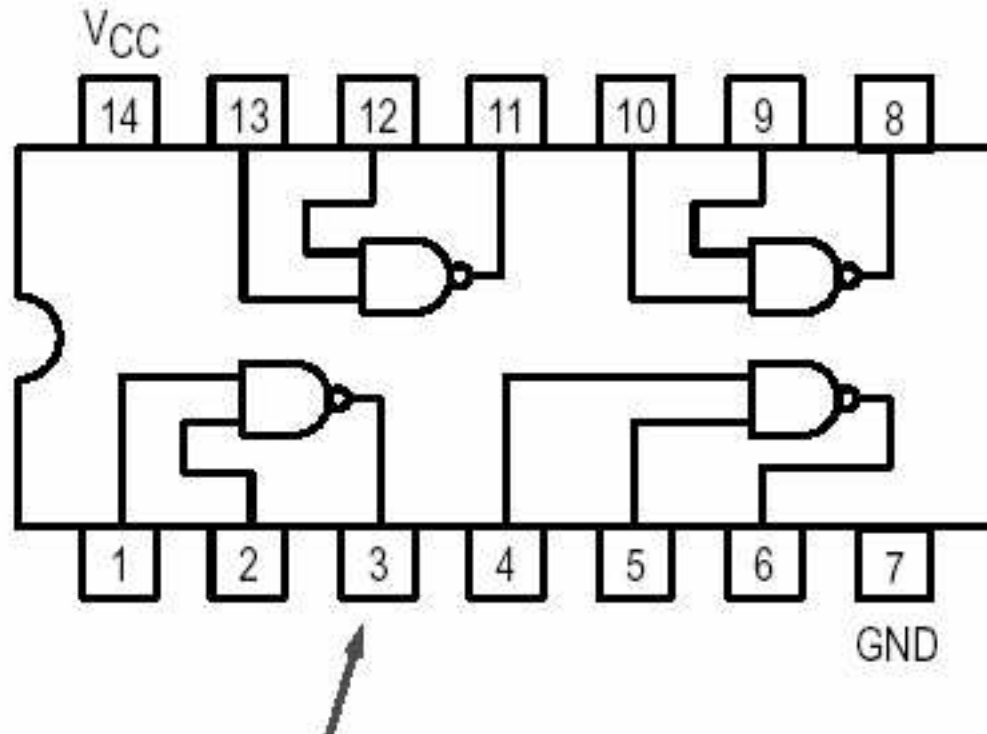

Pin spacing is 0.1" x 0.3"; chip is about 15mm long



- 74LS00 - has four 2-input NAND gates
- Small scale integration (SSI)

Integrated circuits

- Scales of integration
- (Small) SSI: 1-10 gates
- (Medium) MSI: 10-100 gates
- (Large) LSI: 100-100.000 gates
- (Very Large) VLSI: > 100.000 gates

Equivalent Functions

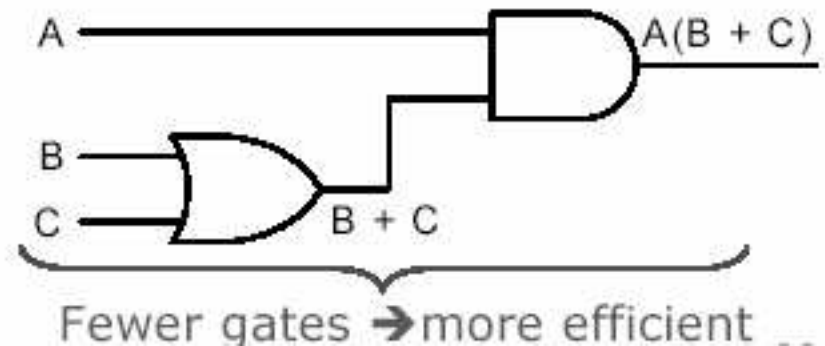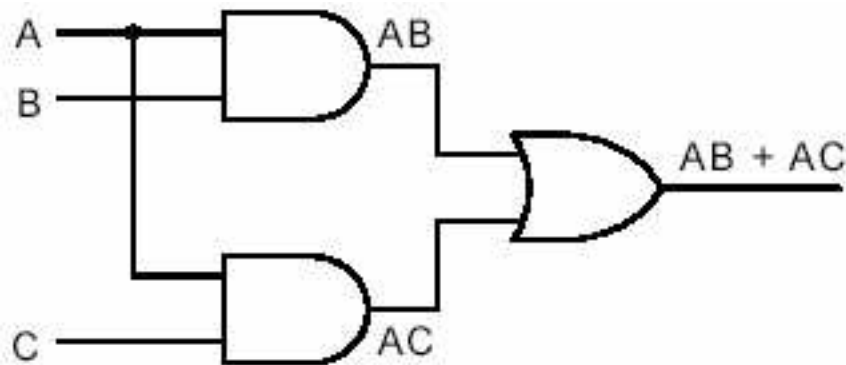- Sum of products (or product of sums) is not necessarily the more efficient form
- Manipulate boolean function to give an equivalent function
- Example: $M = AB + AC = A(B+C)$



Minimization procedures

- Karnaugh's maps (by hand)
- Used to minimize boolean functions of up to 4-5 input variables
- For more variables use the method of Quine-McKluskey (programmable)

Karnaugh's Maps (KM)

- Grid-like representation for boolean functions
- Minterms with just one variable different occupies adjacent cells
- Consider only 1s in the representation (focusing on a SOP representation)
- IDEA: if 2 adjacent cells have a 1 the function can be simplified

A KM for 2-variable functions

- The generic KM

$X \backslash Y$	0	1
0	$\bar{X}\bar{Y}$	$\bar{X}Y$
1	$X\bar{Y}$	XY

- Function $F = XY$

$X \backslash Y$	0	1
0		
1		1

- Function $F = X + Y$


$X \backslash Y$	0	1
0		1
1	1	1

A KM for 3-variable functions


		YZ		Y	
		00	01	11	10
X	0	$\bar{X}\bar{Y}\bar{Z}$	$\bar{X}\bar{Y}Z$	$\bar{X}YZ$	$\bar{X}Y\bar{Z}$
	1	$X\bar{Y}\bar{Z}$	$X\bar{Y}Z$	XYZ	$XY\bar{Z}$
		Z			

An example



- $F = XY'Z + XY'Z' + X'YZ + X'YZ'$

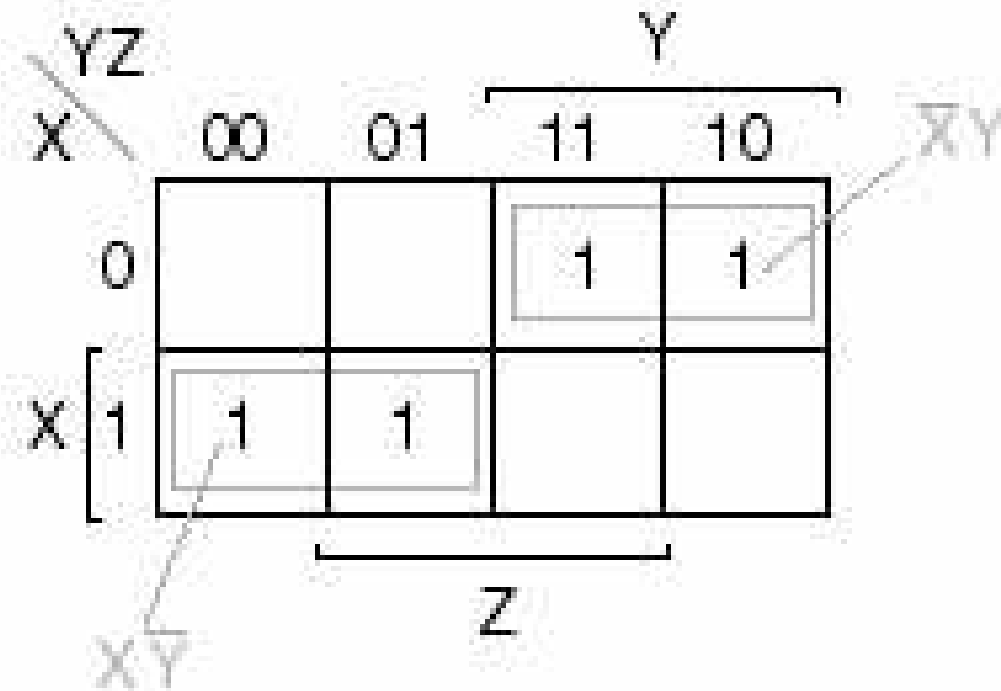

Circular adjacencies for 3 variables

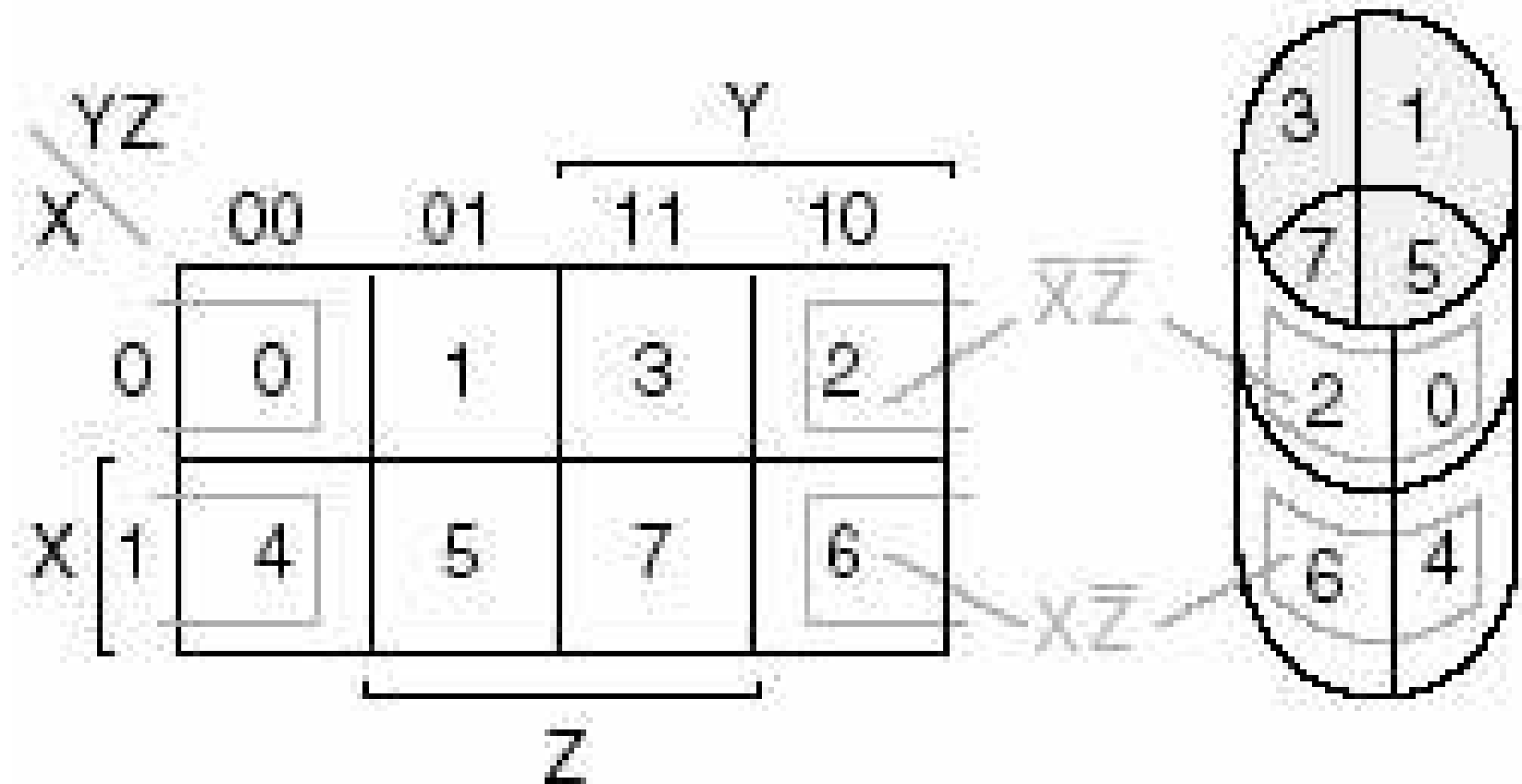

Four 1 adjacents

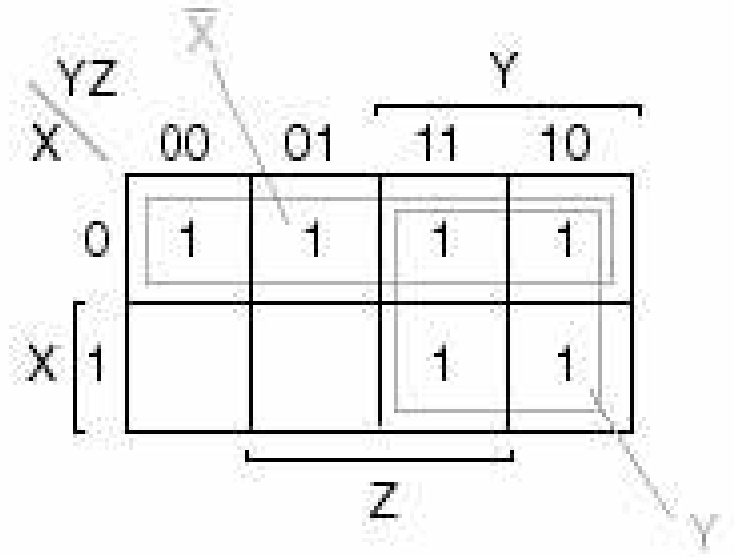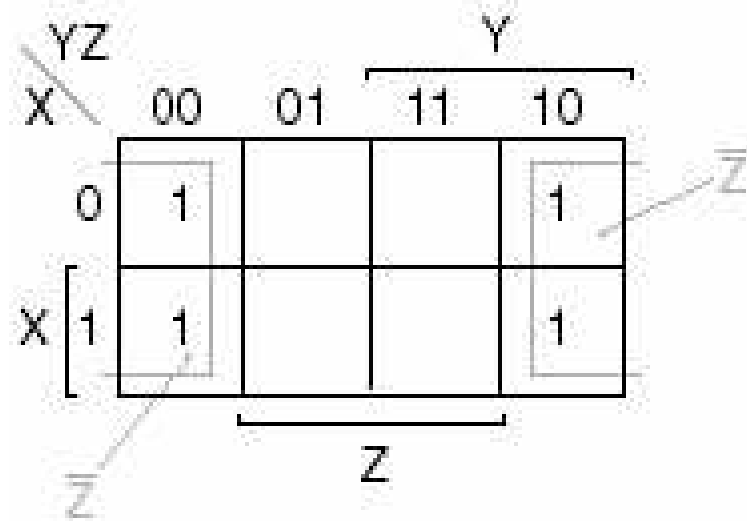

Exercise (1)

- Which is the minimal function $F1$ for this KM?

		YZ			
		00	01	11	10
X	0			1	
	1	1		1	1

Annotations: A bracket above the columns 11 and 10 is labeled Y . A bracket below the columns 01, 11, and 10 is labeled Z .

Solution

- $F1 = YZ + XZ'$

Exercise (2)

- Which is the minimal function F_2 for this KM?

YZ		Y			
		11	10		
X		00	01	11	10
0	1				1
1	1	1			1

Z

Solution

- $F2 = Z' + XY'$

k-cube of 1s

- Is a set of 2^k adjacent cells in k dimensions, where at most k variables change value
- 0-cube, 1 cell, a minterm
- 1-cube, 2 adjacent cells
- 2-cube, 4 adjacent cells
- 3-cube, 8 adjacent cells
-

Prime implicants

- $F = P_1 + P_2 + P_3 + \dots$
- A k -cube is also called an **implicant**
 - Infact, it is a term P_n which implies the function F ,
 - i.e. if P_n is *true* then F is *true*
- A k -cube is a **prime implicant for F** if it does not imply any other implicant of F

Minimal representation

- A prime implicant can be chosen by selecting a k -cube in the KM which is not contained in a larger h -cube (**maximal k -cube**)

- $F = P_1 + P_2 + P_3 + \dots$

has a **minimal representation** if:

1. Each P_n is a prime implicant
2. There is a minimum number of them

Minimality procedure

1. Find maximal k -cubes (prime implicants)
2. If a 1 is covered by only one maximal k -cube this has to be chosen (**essential** prime implicants)
3. Select a minimum number of the remaining k -cube so to cover all 1s not covered by essential prime implicants

Exercise (3)

- Which is the minimal function $F3$ for this KM?

YZ $X \backslash$		Y			
		00	01	11	10
0			1	1	
1		1	1		1

Z

Exercise (4)

- Which is the minimal function F_4 for this KM?


$\begin{array}{c} YZ \\ X \end{array}$		Y			
		00	01	11	10
X	0		1	1	1
	1		1	1	

Z

Solutions

- $F3 = X'Z + XY' + XZ' = Y'Z + XZ' + X'YZ$
- $F4 = Z + X'Y$


A KM for 4-variable functions

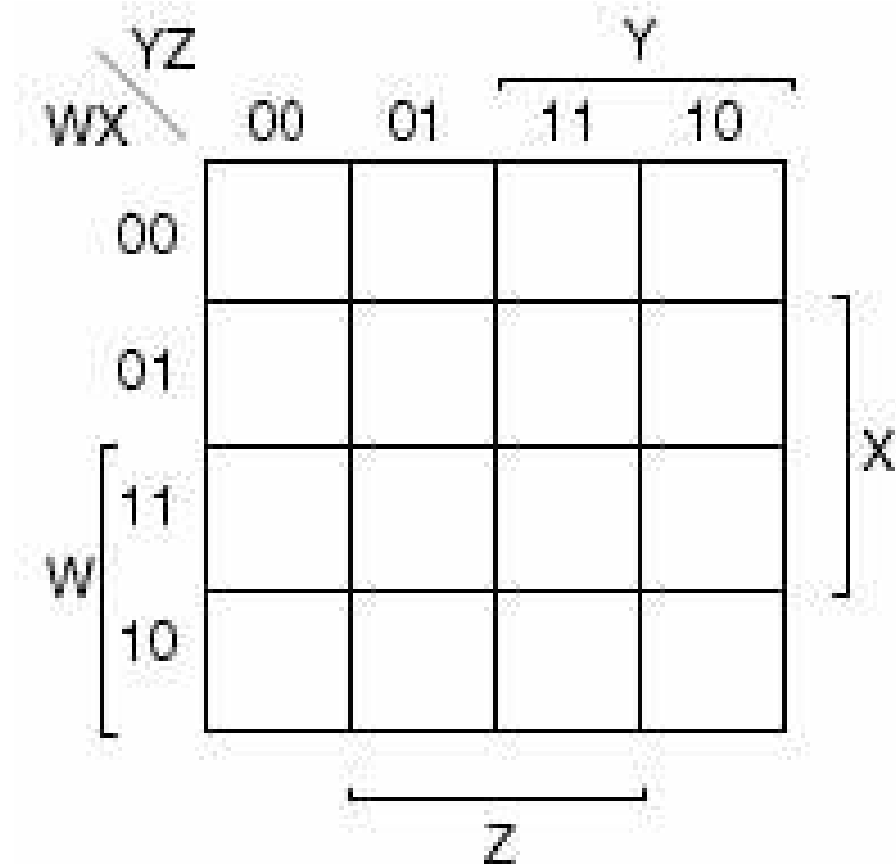

Circular adjacencies for 4 variables


		Y				
		YZ		11	10	
W	WX	00	01	11	10	X
	00	0	1	3	2	
	01	4	5	7	6	
	11	12	13	15	14	
	10	8	9	11	10	Z

\overline{XZ}

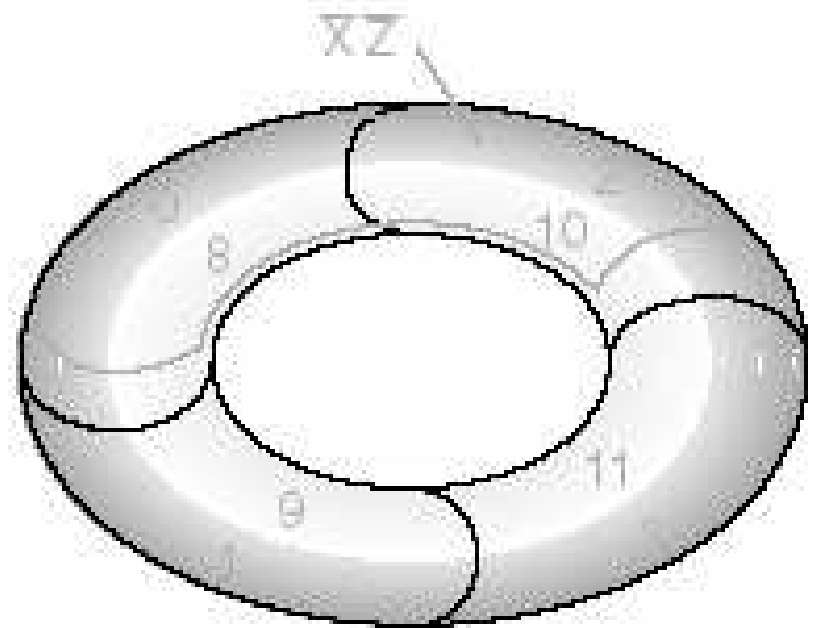

A simple example (1)

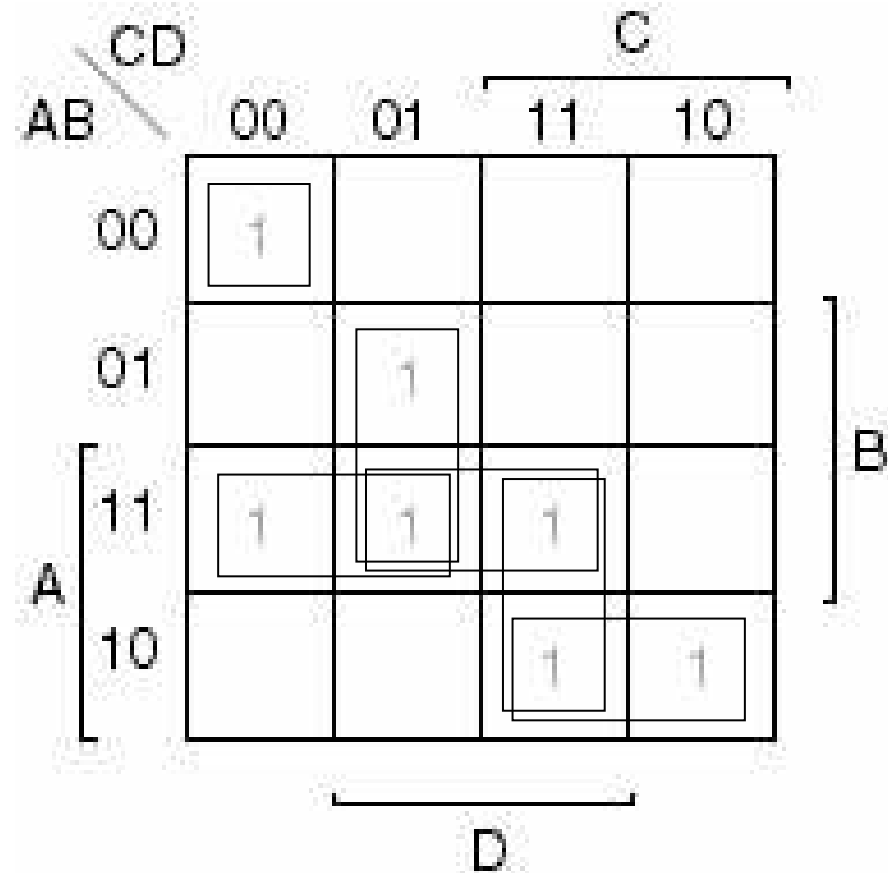- All prime implicants are shown
- Find the essential ones



A simple example (2)

		CD		C	
		00	01	11	10
AB	00	1			
	01		1		
	11	1	1	1	
	10			1	1

A

B

D

More exercise (1)

- Which is the function G1 for this KM?

		YZ			
		00	01	11	10
WX	00	1	1		1
	01	1	1		1
	11	1	1		1
	10	1	1		

Diagram illustrating a Karnaugh Map (KM) for a 4-variable function. The map is a 4x4 grid with rows labeled WX and columns labeled YZ. The columns are grouped by Y (00, 01, 11, 10) and the rows are grouped by X (00, 01, 11, 10). The function G1 is represented by the 1s in the cells where WX is 00, 01, 11, 10 and YZ is 00, 01, 10. The 1s are circled, indicating the function G1 is the sum of the minterms corresponding to these cells.

More exercise (2)

- Which is the function G2 for this KM?

AB \ CD		C			
		00	01	11	10
A	00	1	1		1
	01				1
	11				
	10	1	1		1

Diagram illustrating a Karnaugh Map (KM) for a function G2. The map is a 4x4 grid with rows labeled AB (00, 01, 11, 10) and columns labeled CD (00, 01, 11, 10). The map is partitioned into four 2x2 quadrants labeled A, B, C, and D. The function G2 is defined by the cells containing '1'.

Cells containing '1':

- Row 00: Columns 00, 01, 10
- Row 01: Column 10
- Row 10: Columns 00, 01, 10

More exercise (3)

- Which is the function G3 for this KM?

AB \ CD	00	01	11	10
00		1	1	
01	1	1	1	1
11	1			1
10				

Answers

- $G1 = Y' + W'Z' + XZ'$
- $G2 = B'C' + B'D' + A'CD'$
- $G3 = A'D + A'B + BD'$

The KM method for POS

- Which is the POS expression of function F represented by this KM?

AB \ CD	00	01	11	10
00	1	1	0	1
01	0	1	0	0
11	0	0	0	0
10	1	1	0	1

Solution

- Use the same method used for build POS canonical form from truth tables
- $F = (CD)' \cdot (BD')' \cdot (AB)'$
 $= (C' + D') \cdot (B' + D'')$
 $= (C' + D') \cdot (B' + D) \cdot (A' + B')$

Don't care values

- A *don't care* value in a truth table means indifference for the actual value of the function
 - Truth table on the left may be substituted by anyone on the right

A	B	F
0	0	0
0	1	1
1	0	1
1	1	dc

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

Don't care values in KMs

- Simplify the choice, since each of them (X) can be considered a 0 or a 1

AB \ CD	00	01	11	10
00	X	1	1	X
01	0	X	1	0
11	0	0	1	0
10	0	0	1	0

An alternative choice

- Previous choice gives $F = CD + A'B'$ but a different choice is possible $F = CD + A'D$

A 4x4 Karnaugh map for a function of four variables A, B, C, and D. The rows are labeled AB (00, 01, 11, 10) and the columns are labeled CD (00, 01, 11, 10). The map contains 1s in the following cells: (00,01), (00,11), (01,11), (11,11), (10,11). There are also 'X' marks in the cells (00,00) and (01,01). Three groupings are shown: a horizontal group 'CD' covering columns 01 and 11; a vertical group 'A'D' covering rows 00 and 10 in column 11; and a square group 'A'B'' covering rows 00 and 01 in column 01. Brackets labeled A, B, C, and D indicate the variable ranges for the groups.

AB \ CD	00	01	11	10
00	X	1	1	X
01	0	X	1	0
11	0	0	1	0
10	0	0	1	0