

# **Enrico Nardelli**

# **Logic Circuits and**

# **Computer Architecture**

---

## **Appendix A**

## **Digital Logic Circuits**

### **Part 2:     Combinational and**

### **Sequential Circuits**

# Combinational circuits

---




- Each of the  $m$  outputs can be expressed as function of  $n$  input variables
- Truth table has:
  - $n$  input columns
  - $m$  output columns
  - $2^n$  rows (all possible input combinations)

# Multiplexer (Mux)

---

- $2^n$  data inputs -- 1 output
- $n$  controls, to select one of the inputs to be "sent" to the output

Example: 4-to-1 mux

 


Logic symbol

Truth table

$S_1$	$S_0$	F
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

# Logic circuit for a 4-to-1 Mux

---

 


Rev. 4.1 (2006-07) by Enrico Nardelli

# Exercise

---

- Consider a 2-to-1 multiplexer:
  - 2 data inputs:  $D_0$  and  $D_1$
  - 1 control input:  $S_0$
  - 1 data output:  $F$
- Write
  - Truth table
  - Logic circuits which implements it
- Extend it to deal with 4 bits at a time

# Quadruple 2-to-1 mux

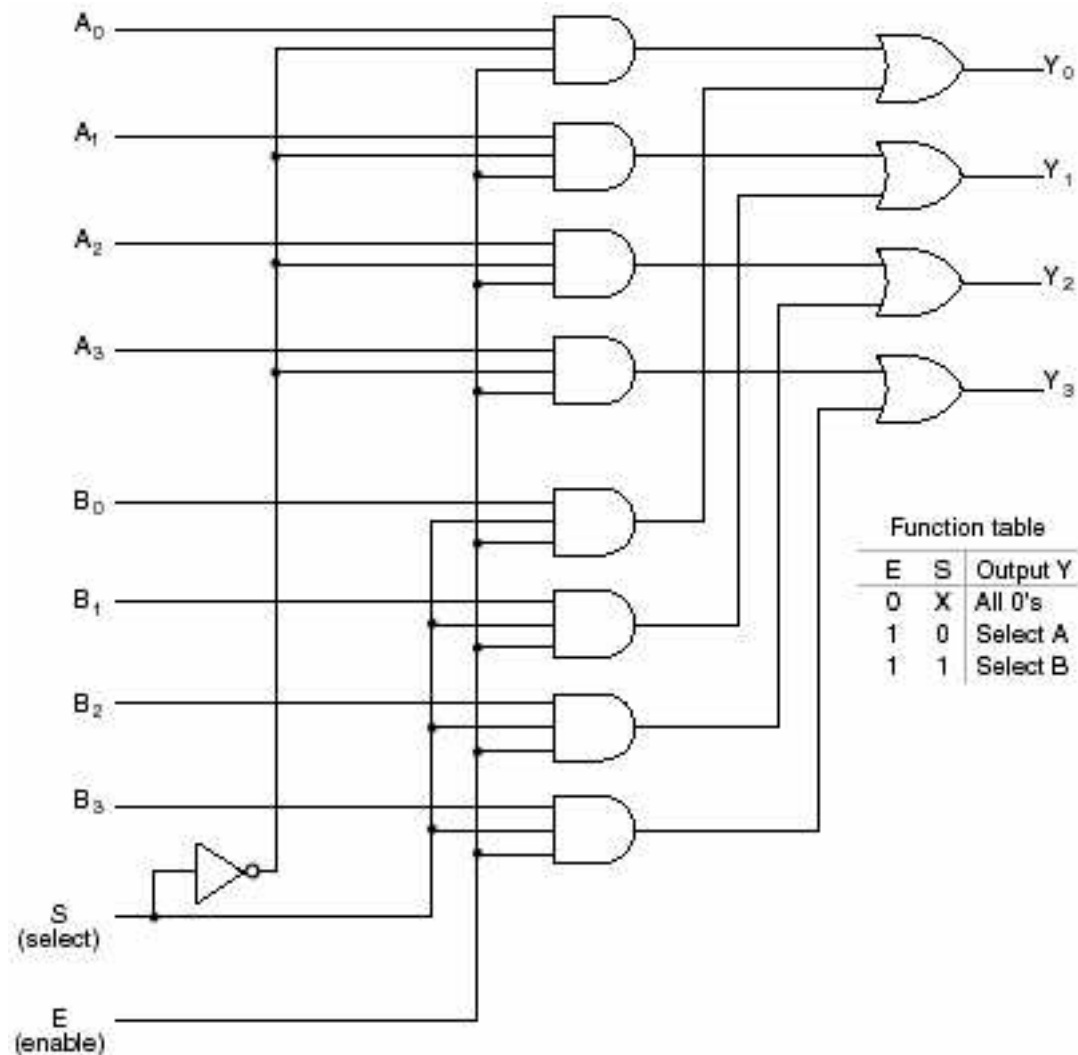

# De-multiplexer (Demux)

---

- 1 input --  $2^n$  data outputs --
- $n$  controls, to select exactly one of the outputs to “receive” the input

Example: 1-to-4 demux

input:  $E$ , controls:  $S_0, S_1$


outputs:  $D_0, D_1, D_2, D_3$

$S_0$	$S_1$	$D_0$	$D_1$	$D_2$	$D_3$
0	0	E			
1	0		E		
0	1			E	
1	1				E

Truth table

# Logic circuit for a 1-to-4 Demux

---

 




# Decoder

---

- Convert  $n$  inputs to exactly one of  $2^n$  outputs  
i.e., given an  $n$ -bit value  $i$  in input the decoder activates only the  $i$ -th output line
- Example: a 3-to-8 decoder
  - A 3-bit value in input
  - 8 output lines
  - Write the truth table and the logic circuit

# A 3-to-8 decoder

---

 


# Read Only Memories (ROMs)

---

- They are just a combinational circuits !
- A simple example for a 8-cell ROM with 3 bits per cell

$A_0$	$A_1$	$A_2$	$D_0$	$D_1$	$D_2$
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

# The implementation

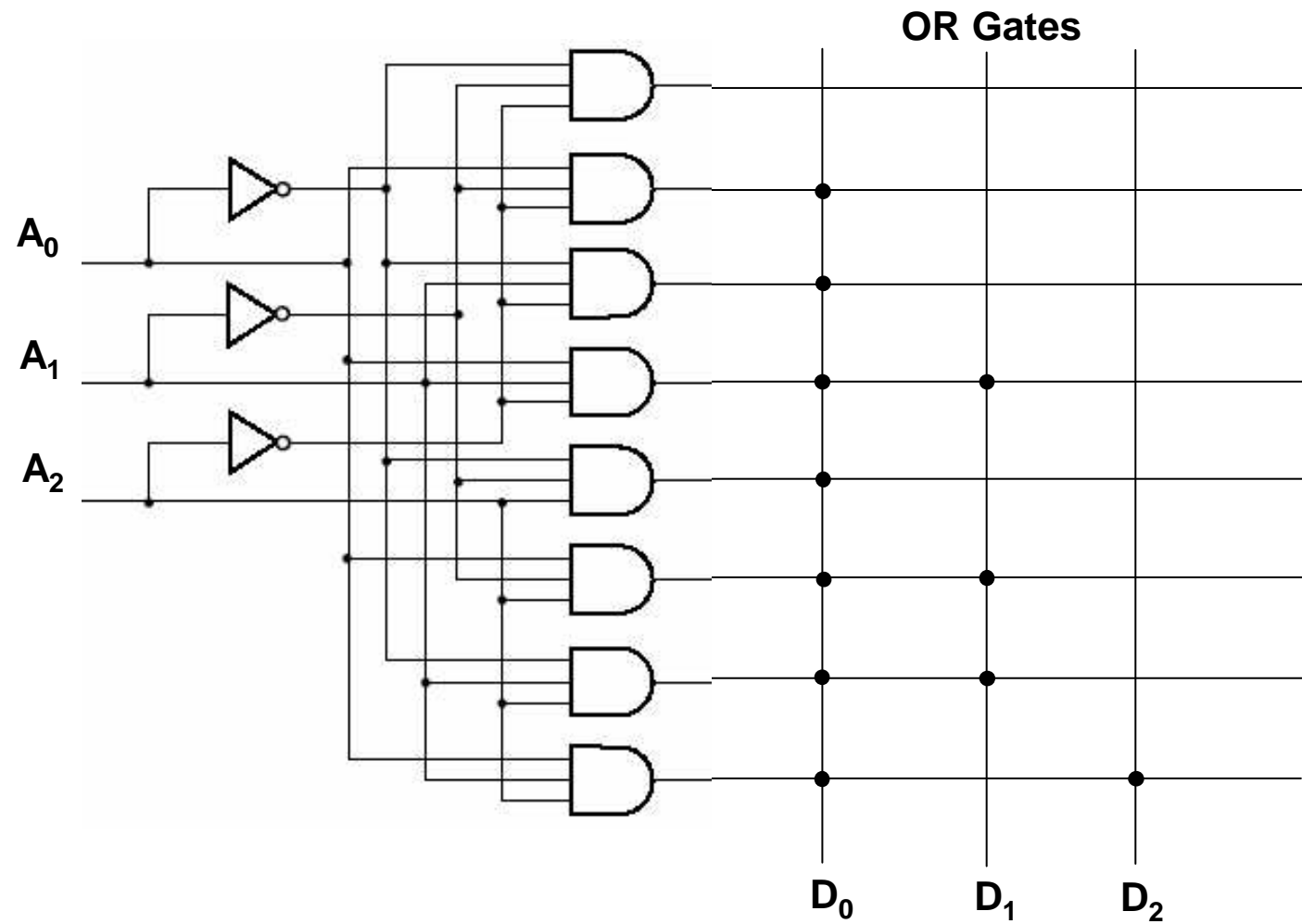

# Exercise

---

- Build a ROM-based combinatorial circuit with
  - INPUT: 3 boolean variables
  - OUTPUT: the number of the 1s in the input


# Solution: Truth Table

---

$A_0$	$A_1$	$A_2$	$D_1$	$D_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Solution: the implementation

---

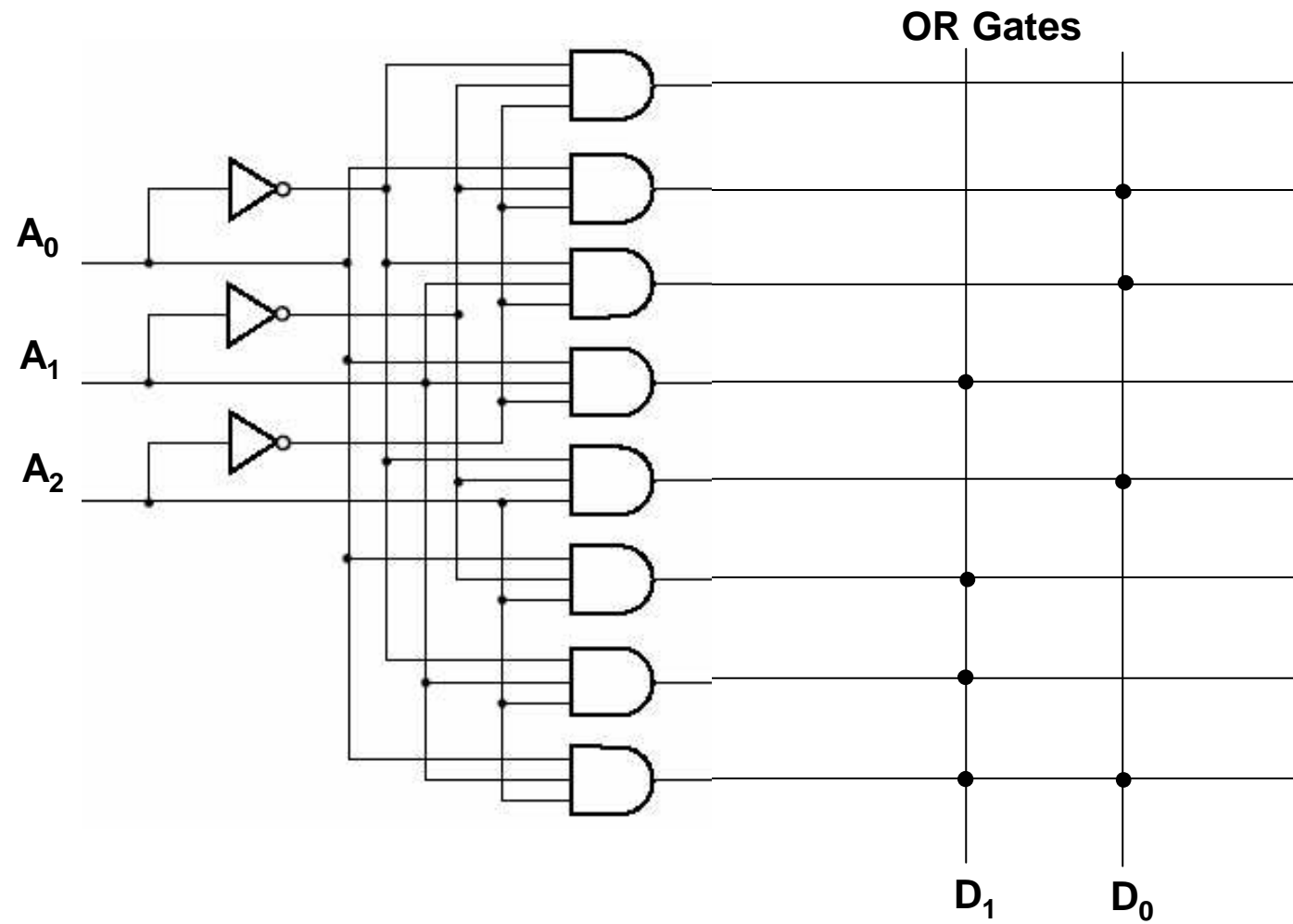

# Binary sum

---

Addend-1	0+	0+	1+	1+
Addend-2	0=	1=	0=	1+
Sum	0	1	1	0
Carry	0	0	0	1

It's just a 2-input, 2-output boolean function !  
Called **half sum** since it ignores the carry-in



# The half adder


---

- Sum two binary inputs without the carry-in

Truth table

X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Logic Circuit

 

# The complete addition

---

- Has to be able to deal with the carry-in

It's called **full adder**

Z represents the carry-in

Truth table

X	Y	Z	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Karnaugh's maps for full adder

		Y			
		YZ		11	10
X	0		1		1
	1	1		1	

Z

$$\begin{aligned}
 S &= X'Y'Z + X'YZ' + XY'Z' + XYZ \\
 &= X \oplus Y \oplus Z
 \end{aligned}$$


		Y			
		YZ		11	10
X	0			1	
	1		1	1	1

Z

$$\begin{aligned}
 C &= XY + XZ + YZ \\
 &= XY + XY'Z + X'YZ \\
 &= XY + Z.(XY' + X'Y) \\
 &= XY + Z.(X \oplus Y)
 \end{aligned}$$

# The logic circuit of a full adder


---

 
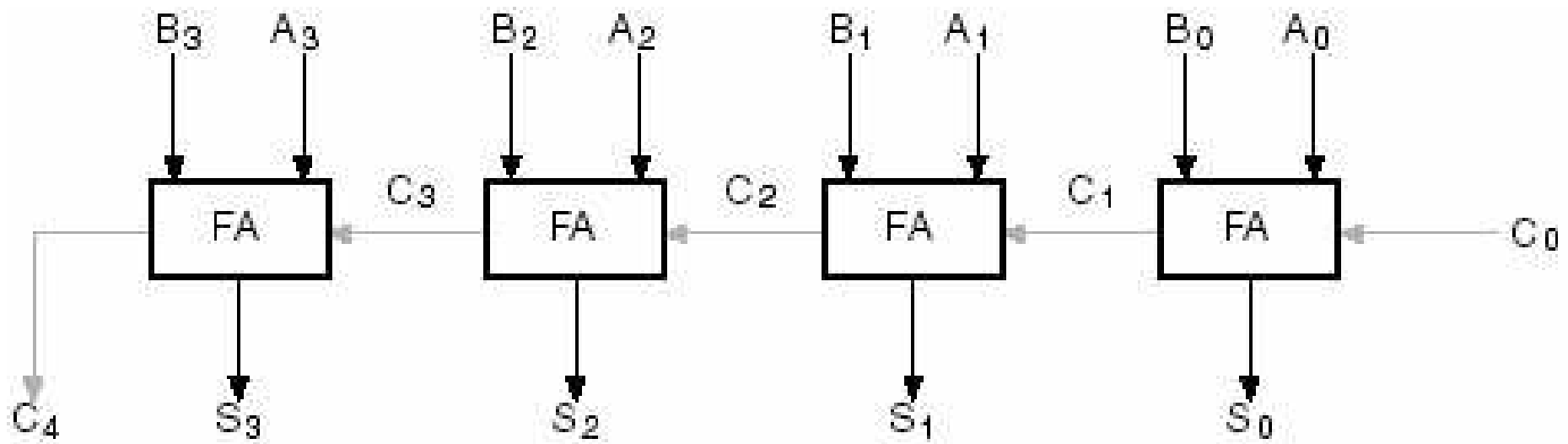
# Binary adder

---



- Has to be able to deal with more bits
- An  $n$ -bit adder can be built chaining  $n$  full adders
- It's called **ripple-carry** adder



# Ideal behaviour of circuits

---


- Consider an inverter (NOT gate)

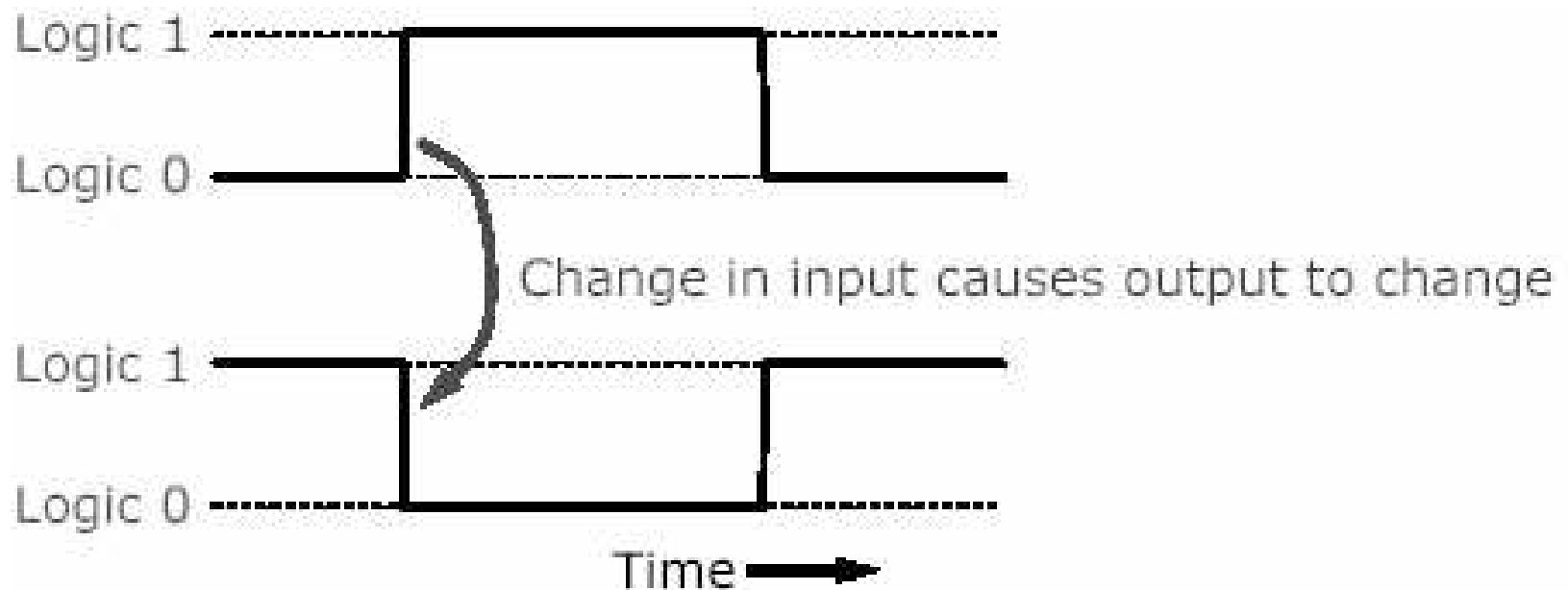 
 
# The real behaviour

---

- Propagation delay: time needed for a change in the input to affect the output (**gate delay**)
- Fall time: time taken for the signal to fall from high level to low level
- Rise time: time taken to rise from low to high



# Carry Propagation

---

- Signals must propagate from inputs for output to be valid
- Carry and sum outputs of a single full-adder are valid  $c$  “gate-delays” after inputs are stable
- Value of  $c$  depends on the used technology
- In a binary adder of  $n$  bits the last carry is valid  $c \cdot n$  “gate-delays” after inputs are stable
- For  $n$  large it may be unacceptable !



# Solution

---

- Pre-compute all carry-ins:
  - **carry look-ahead** adder
- Write a general expression for a carry
  - When does an input carry propagates to the output?
  - When is a carry generated in the output?

x	y	z	s	c
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# General expression

---

- General expression for the  $(i+1)$ -th carry
  - $c_{i+1} = x_i y_i + c_i (x_i + y_i) = g_i + c_i p_i$
  - $g_i \rightarrow$  generate carry
  - $p_i \rightarrow$  propagate carry
  - Iterate the expression for  $c_{i+1}$

## General expression (2)

---

$$\begin{aligned}c_{i+1} &= g_i + p_i(g_{i-1} + c_{i-1}p_{i-1}) = g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-1} = \\&= g_i + p_i g_{i-1} + p_i p_{i-1} (g_{i-2} + c_{i-2} p_{i-2}) \\&= g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} + p_i p_{i-1} p_{i-2} c_{i-2} \\&= g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} + p_i p_{i-1} p_{i-2} g_{i-3} + p_i p_{i-1} p_{i-2} p_{i-3} g_{i-4} + \dots\end{aligned}$$


- It could be developed until the least significant input bits
- Every  $c_i$  depends only on  $c_0, p_j, g_j$  ( $j < i$ )

# Carry expressions for a 4-bit adder

---

- $c_1 = g_0 + p_0c_0$
- $c_2 = g_1 + p_1g_0 + p_1p_0c_0$
- $c_3 = g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0$
- $c_4 = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0c_0$

# Carry Look-Ahead: the architecture

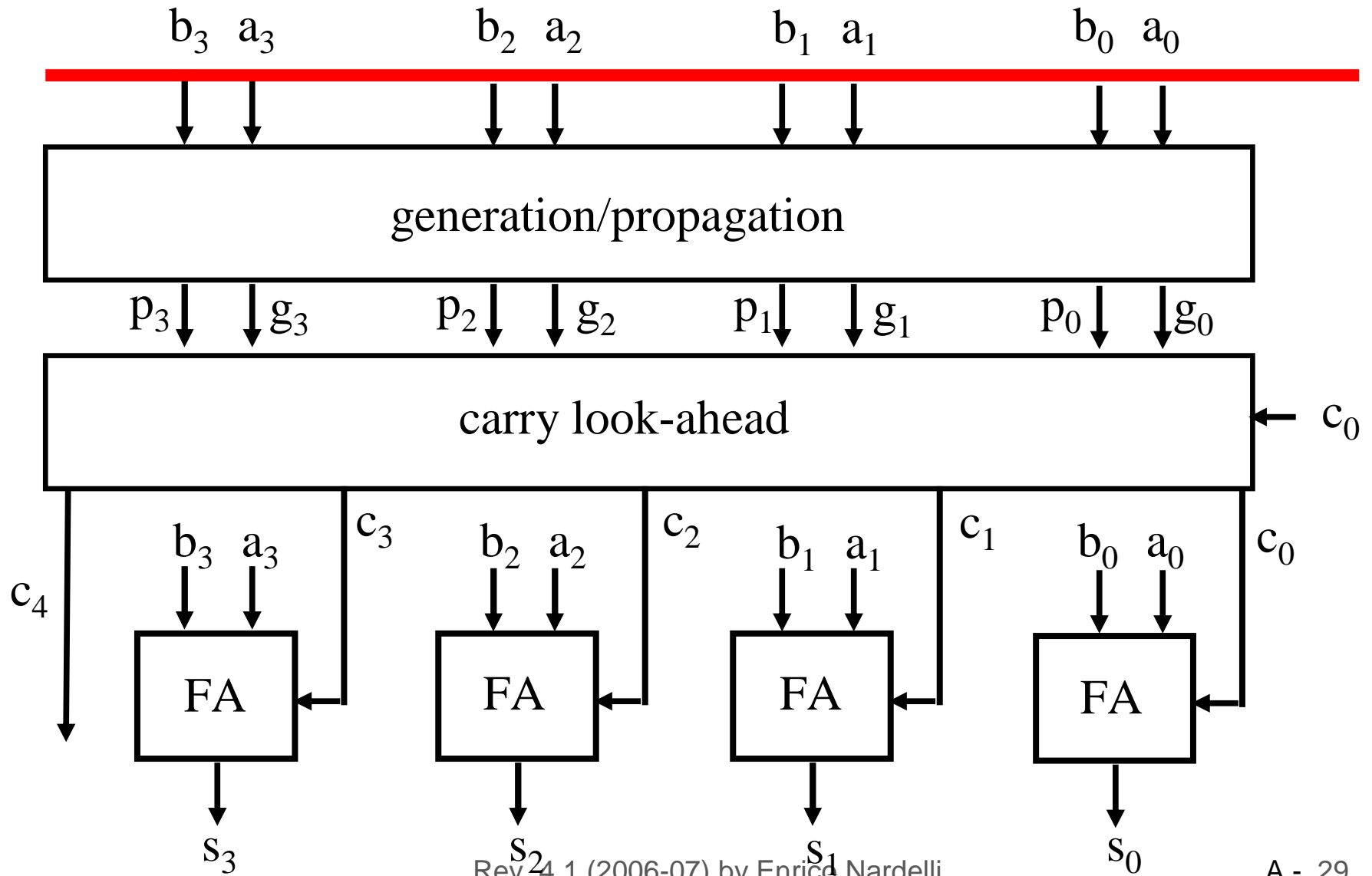

# A practical problem

---

- $c_1 = g_0 + p_0 c_0$
- $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
- $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$
- $c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$

there is a limit due to circuit **fan-in**:  
the maximum number of inputs


# Practical solution for $n$ bits

---

- Use carry look-ahead adders for just  $m$  consecutive bits (4-8 is typical)
- Each of these is a *stage*
- Use  $n/m$  stages connected by means of the ripple-carry technique
- The overall delay is now only  $c \cdot n/m$  "gate delays"

# A mixed solution

---

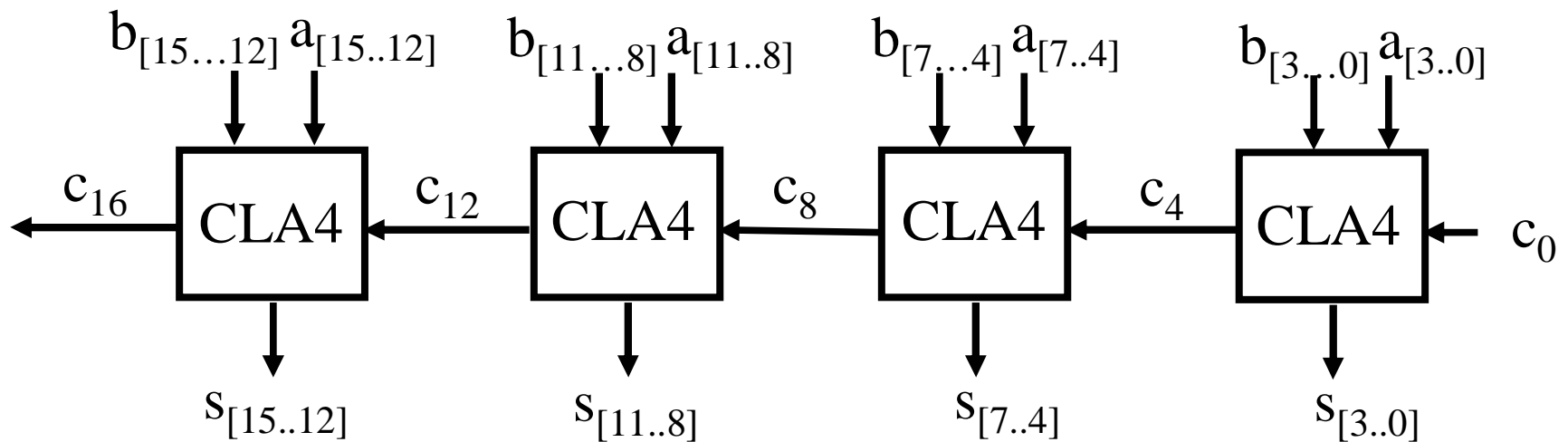



# Sequential circuits



---

- More difficult to analyze since there is **feedback**: output is *fed back* to input
- Need to introduce a concept of state
  - **Current** state and **next** state
- **Asynchronous**: change of state of an element is fed into other elements without any coordination
- **Synchronous**: change of state of each element is fed into other elements only at a given instant, the same for all elements

  
# Initial examples

---

- What does this circuit do ?
- What about this one ?



These are  
the same  
circuits

 


- Replace inverters with NOR gates
 
# SR-Latch

---

- Analyze this circuit (write truth table)



# Analysis of SR-Latch

---

- Two kinds of analysis
- COMBINATIONAL
  - Consider all possible configurations of S,R,Q and check their feasibility
- SEQUENTIAL
  - Consider all possible configurations of S,R,Q at a generic step  $k$  and check what happens for Q at step  $k+1$

# SR-Latch Truth Table: Combinational View

---

- 8 possible combinations ( $Q = \text{NOT } Q'$ )

#	S	R	Q	Q'	name
0	0	0	0	1	Keep
1	0	0	1	0	Keep
2	0	1	0	1	Reset
5	1	0	1	0	Set
7	1	1	1	0	Unfeasible combination
3	0	1	1	0	Unfeasible combination
4	1	0	0	1	Unfeasible combination
6	1	1	0	1	Unfeasible combination

# SR-Latch Truth Table: Sequential View

---

- Next state as a function of current state

#	S	R	Q(k)	Q(k+1)	Q'(k+1)	<i>name</i>
0	0	0	0	0	1	Keep (stable)
1	0	0	1	1	0	Keep (stable)
2	0	1	0	0	1	Reset (stable)
3	0	1	1	0	1	Reset ( <i>transient</i> )
5	1	0	1	1	0	Set (stable)
4	1	0	0	1	0	Set ( <i>transient</i> )
6	1	1	0	0	0	<i>Transient but unacceptable !</i>
7	1	1	1	0	0	<i>Transient but unacceptable!</i>

# First reason to avoid $S=R=1$

---

- When both inputs go from 1 to 0:
  - a **race** condition happens
- Both outputs are driven from 0 to 1
- Due to unpredictable physical differences one of the NOR gates may commute earlier from 0 to 1
- Then it will prevent the commutation of the other gate
- Conclusion: output value is unpredictable !

# Second reason to avoid $S=R=1$


---

- When both inputs go from 1 to 0:
  - a **race** condition happens
- Both outputs are driven from 0 to 1
- Both the NOR gates commute from 0 to 1 almost at the same time
  - This drives both outputs from 1 to 0
  - Both gates are again forced to commute
  - This repeats again and again
- Conclusion: output values oscillate !



# Temporal evolution of SR-latch

---

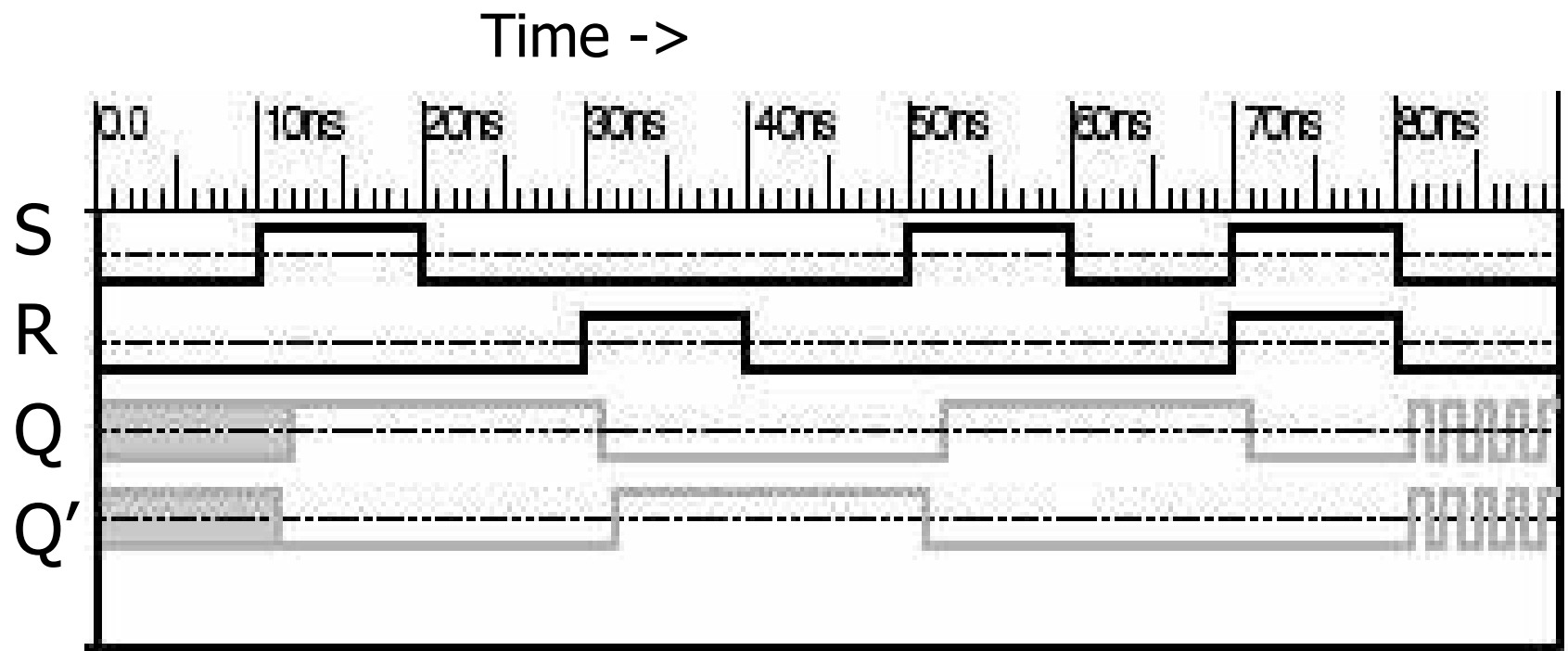

# Adding a clock to SR-latch


---

- An additional input (the **clock**) is used to ensure the latch commutes only when required

pulses of a clock



 
- The latch senses S and R only when Clock=1


 
# The role of the clock



---

- A clock ensures commutation is propagated from the input to the output only when required
- But the general system clock is running continuously: how can it be used to control a circuit only when needed?



# Circuit clock from system clock

---

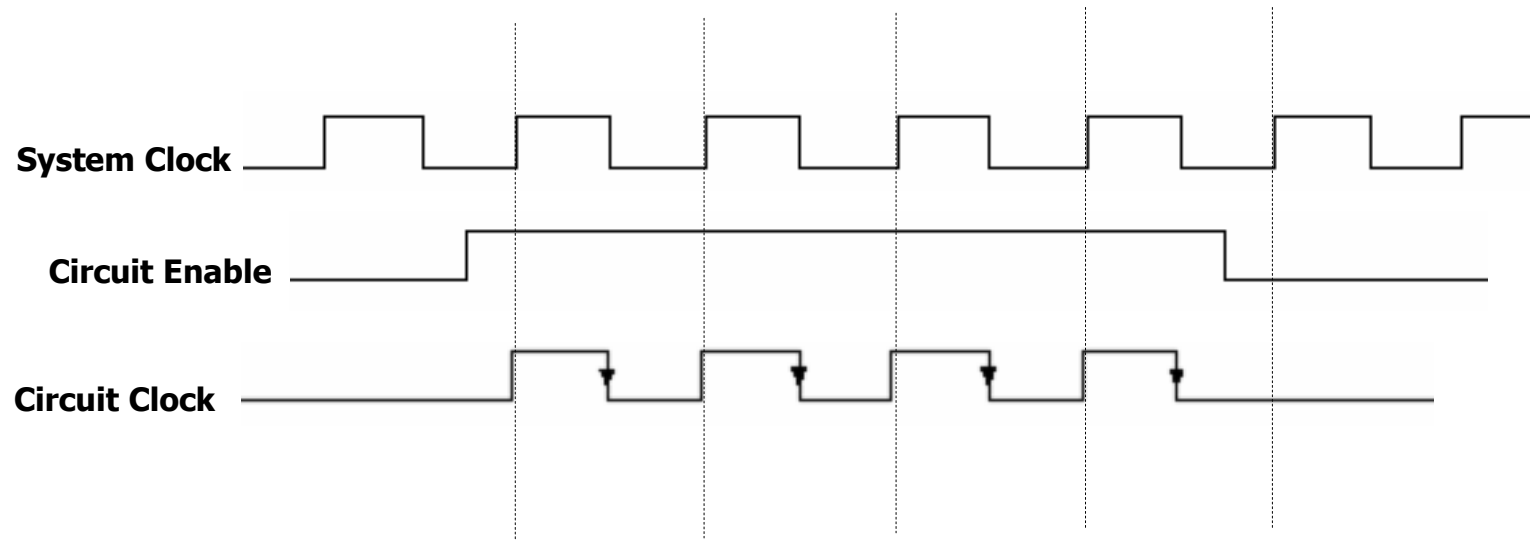 

# A more subtle problem

---

- Even if the circuit is clocked, inputs to the internal NOR gates receiving S and R may arrive with different delays
- In a commutation from  $(S=1, R=0)$  to  $(S=0, R=1)$  the SR-latch outputs may be (for some time) in the unacceptable state where both are 0

# Example

---

- The NOR gate receiving the R:0-to-1 input may commute earlier than the other gate and now outputs of the SR-latch are in an unacceptable state

	Initial state	Input change	Transient state	Stable state
S	1	0	0	0
R	0	1	1	1
Q	1	1	0	0
Q'	0	0	0	1

- If Q and Q' are in input to a further circuit, this receives wrong input values, hence its computed output may differ from the required one


# The solution: a Flip-Flop circuit

---

- A 2-stage (*master* and *slave*) circuit
- First the master stage (connected to circuit's inputs only) changes its state (**flip**) when clock commutes to 1
- Then the slave stage (connected to circuit's outputs only) reads master's outputs after they have stabilized, when clock commutes to 0, and changes its state (**flop**)
- The next circuit will read slave's outputs in the next clock commutation to 1, when they have stabilized
- Outputs from the  $i$ -th circuit are read in input to the  $(i+1)$ -th circuit only after the transient unacceptable phase is ended, since adjacent stages are "active" only during different half periods of the clock
- In a chain of circuits this allows to control exactly when the (commuted) output of the  $i$ -th circuit acts on the input of the  $(i+1)$ -th circuit

# SR flip-flop

---

 



# How SR flip-flop solve the problem


- Temporal evolution (both stages have a transient phase, but its effect on the next stage are hidden):

	In.	$S\uparrow$	$C\uparrow$	c1	$C\downarrow$	c2	SR	$C\uparrow$	Tr.	c1	$C\downarrow$	Tr.	c2
S	0	1	1	1	1	1	0	0	0	0	0	0	0
R	0	0	0	0	0	0	1	1	1	1	1	1	1
C	0	0	1	1	0	0	0	1	1	1	0	0	0
$C'$	1	1	0	0	1	1	1	0	0	0	1	1	1
Y	0	0	0	1	1	1	1	1	0	0	0	0	0
$Y'$	1	1	1	0	0	0	0	0	0	1	1	0	1
Q	0	0	0	0	0	1	1	1	1	1	1	0	0
$Q'$	1	1	1	1	1	0	0	0	0	0	0	0	1
 
# D flip-flop: a secure SR flip-flop

---

- Forcing R to always be NOT(S) the critical condition  $S=R=1$  is avoided




# Use of D flip-flop

---

- A D flip-flop is a memory cell, since it stores what is presented at its input

Symbol

 


Truth table

D	$Q_{n+1}$
0	0
1	1

- Read-Enable (RE) and Write-Enable (WE) signals to store and read values
- Additional Preset (writes 1) and Clear (writes 0) signals to prepare the gate

# 4 bit register

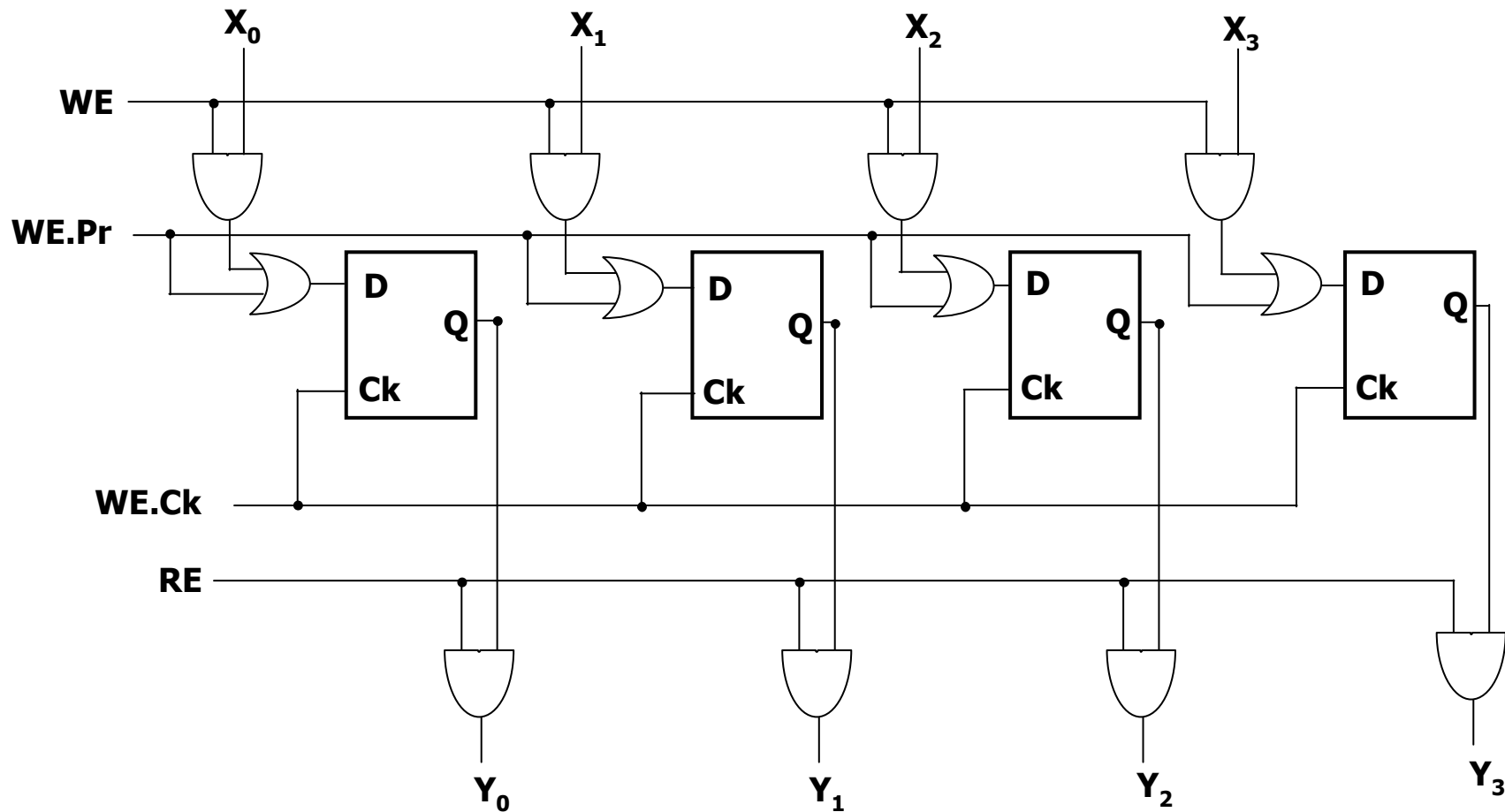


# Use of D flip-flop (2)

---


- A D flip-flop is a delay unit, since it replicates at the output - one propagation delay later - what is presented at its input (delay flip-flop)
- A chain of  $n$  D flip-flops can be used to delay a bit value for  $n$  clock pulses

# 4 bit delay unit

---

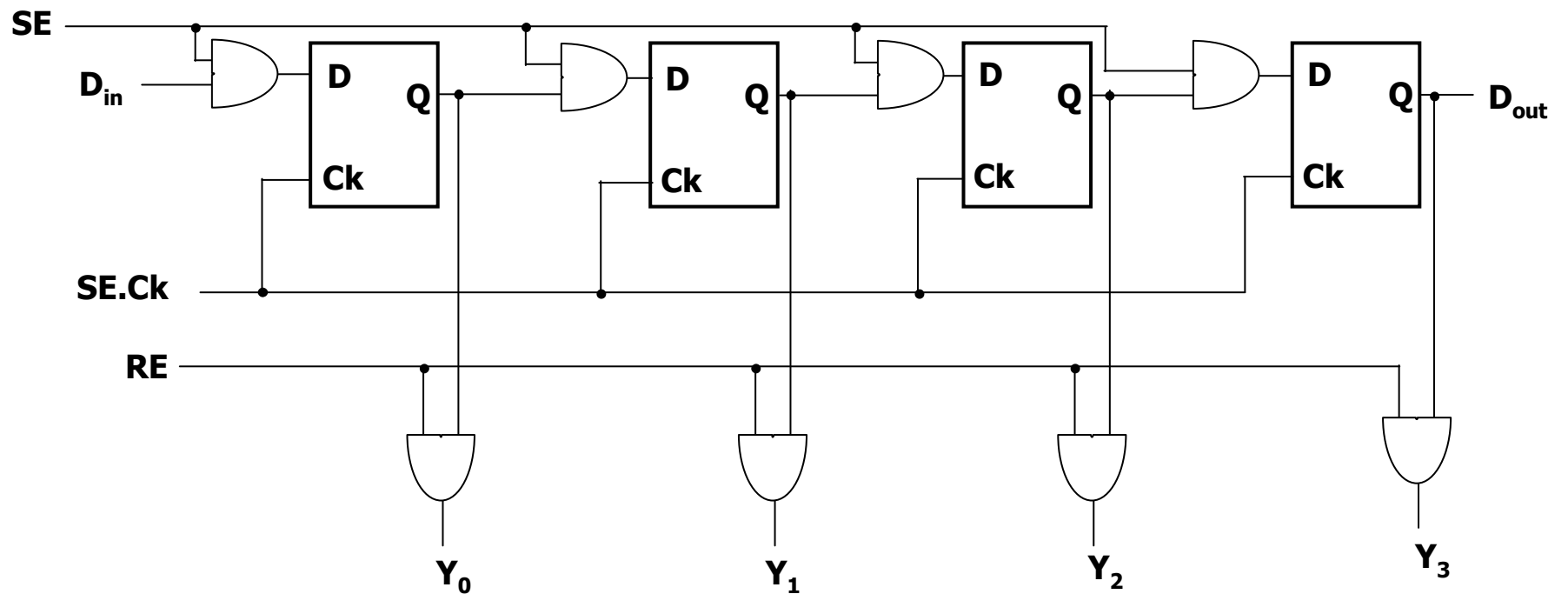

# 4 bit shift register

 

# Register Control Signals


---

- WE (Write Enable): needed since many registers are attached to (i.e., receive data from) the same data bus
- SE (Shift Enable): allows a register output to drive next register input
- RE (Read Enable): needed since many registers are attached to (i.e., put data on) the same data bus



# JK flip-flop: using also $S=R=1$

---

 

# JK flip-flop: temporal evolution (1)

		J↑	C↑	C↓	J↓	C↑	C↓	K↑	C↑	C↓	J↑	C↑	C↓	C↑	C↓
J	0	1	1	0	0	0	0	0	0	0	1	1	1	1	1
K	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
Q	0	0	1	1	1	1	1	1	1	0	0	0	1	1	0
Q'	1	1	0	0	0	0	0	0	0	1	1	1	0	0	1
JQ'=S	0	1	1	0	0	0	0	0	0	0	1	1	0	0	1
KQ=R	0	0	0	0	0	0	0	1	1	0	0	0	1	1	0
Y	0	0	1	1	1	1	1	1	0	0	0	1	1	0	0
Y'	1	1	0	0	0	0	0	0	1	1	1	0	0	1	1

- Sequence of events



# JK flip-flop: temporal evolution (2)

		J↓ K↓	C↑	C↓	K↑	C↑	C↓	J↑ K↓	C↑	C↓	K↑	C↑	C↓		C↑	C↓
J	1	0	0	0	0	0	0	1	1	1	1	1	1		1	1
K	1	0	0	0	1	1	1	0	0	0	1	1	1		1	1
Q	0	0	0	0	0	0	0	0	0	1	1	1	0		0	1
Q'	1	1	1	1	1	1	1	1	1	0	0	0	1		1	0
JQ'=S	1	0	0	0	0	0	0	1	1	0	0	0	1		1	0
KQ=R	0	0	0	0	0	0	0	0	0	0	1	1	0		0	1
Y	0	0	0	0	0	0	0	0	1	1	1	0	0		1	1
Y'	1	1	1	1	1	1	1	1	0	0	0	1	1		0	0

- Sequence of events



# Tabular description for JK-FF

---

- Input: J, K; State: Q; Output: Q

J	K	$Q_n$	$Q_n$
0	0	0	0
0	1	0	0
1	0	0	0
1	1	0	0
0	0	1	1
0	1	1	1
1	0	1	1
1	1	1	1

J	K	$Q_n$	$Q_{n+1}$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1
0	0	1	1
0	1	1	0
1	0	1	1
1	1	1	0

# Transition Tables

---

- Synthetic description of flip-flop dynamics

S	R	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	---


D	$Q_{n+1}$
0	0
1	1

J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$Q'_n$

\_\_\_\_\_


# Temporal behaviour (1)

---

 

# Temporal behaviour (2)


---

 




# Temporal behaviour (3)

---

 


# Temporal behaviour (4)

---

 


# Temporal behaviour (5)

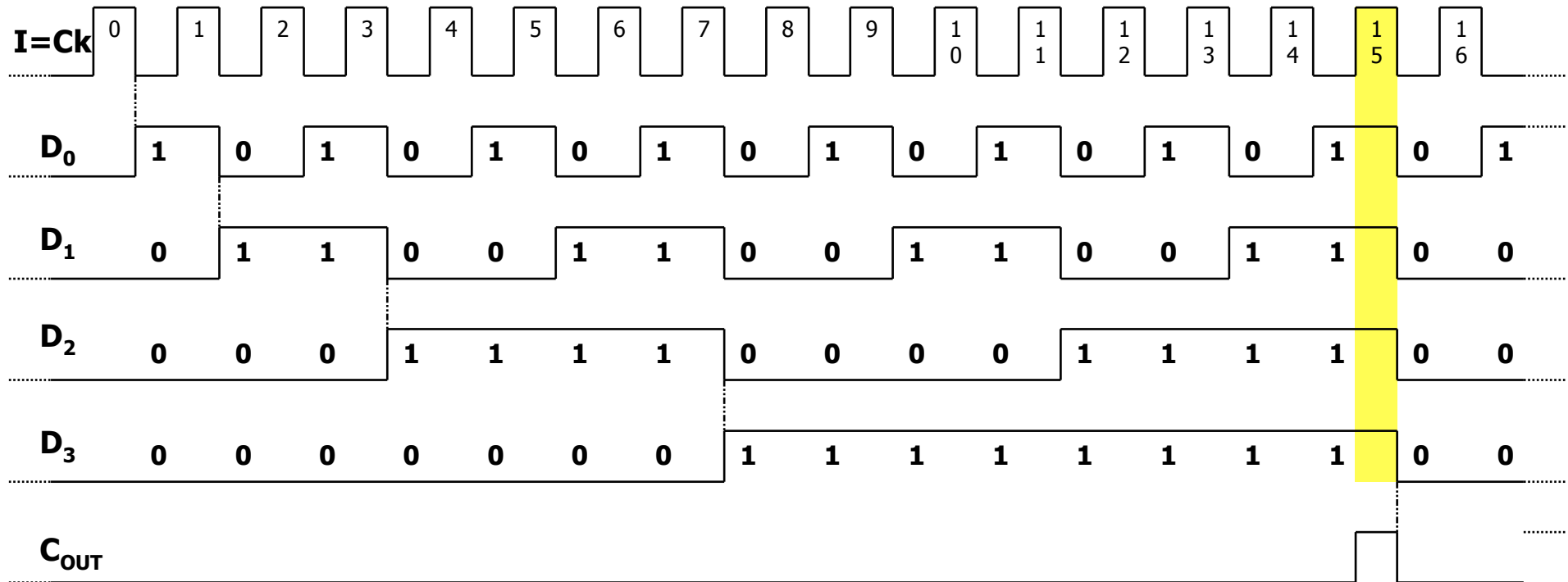
 
# Finite State Machines (FSM)

---


- Called also Finite State Automata (FSA)
- Described by a table of **transitions** between **states** as a consequence of **inputs**
- If an input is true in a given state, a transition changes the state and may produce an **output**
- Graphical representation (states are circles, transition are arrows, input and output are arrow labels):


 
# A very simple example of FSM

---

- When the tank of my car is *full*, if it is an *holiday* I *make a trip*, but if it is a *week-day* I *go to work* by bus. After the trip, the tank is *empty* and when I find a *gas station* I *fill* the tank



# Tabular description for this FSM

---

- Next state as a function of current state and input

Current state	Input	Next state
Tank full	Holiday	Tank empty
Tank full	Week-day	Tank full
Tank empty	Gas station	Tank full

- Output as a function of current state and input

Current state	Input	Output
Tank full	Holiday	Make a trip
Tank full	Week-day	Go to work
Tank empty	Gas station	Fill the tank

# Abstraction process


---

- FSM **describe** sequential networks (SN)
- SN **realizes** Finite State Machines
- The **analysis** of a SN allows to write the corresponding FSM
- From a FSM a SN is obtain through a **synthesis** process
- Similar to boolean functions and logical circuits
  - Boolean Functions (BF) **describe** logical circuits (LC)
  - LC **realize** Boolean Functions
  - The analisys of a LC produces a BF
  - LC are combinational networks (memoryless) synthesizing BF
 
# FSA for D flip-flop

---

- Use Q as state descriptor (**state variable**)
- Use D as input
- Use Q as output
- Check for completeness





# Its tabular description

---

- Output values as a function of input and current state values
- Next state values as a function of input and state value
  - D flip-flop

Output:

D	$Q_n$	$Q_n$
0	0	0
0	1	1
1	0	0
1	1	1


State:

D	$Q_n$	$Q_{n+1}$
0	0	0
0	1	0
1	0	1
1	1	1
 
# FSA for SR flip-flop

---

- Use Q as state variable
- Use S and R as input
- Use Q as output
- Transitions with multiple conditions




- Unacceptable input configurations are NOT represented
 
# FSA for JK flip-flop

---

- Just add condition 11 to existing transitions
- Note stability and instability of states according to input values





# Synthesis of a SN from a FSA

---

- Identify input, output and state variables
- Build (and minimize) truth tables for output variables as a function of input and state values
- Build (and minimize) transition tables for state variables as a function of input and state values
- Decide which FF to use to store state values
  - a D-FF is the simplest choice
  - to store 0 present 0 at the input
  - to store 1 present 1 at the input


# Generic architecture of a SN

---

 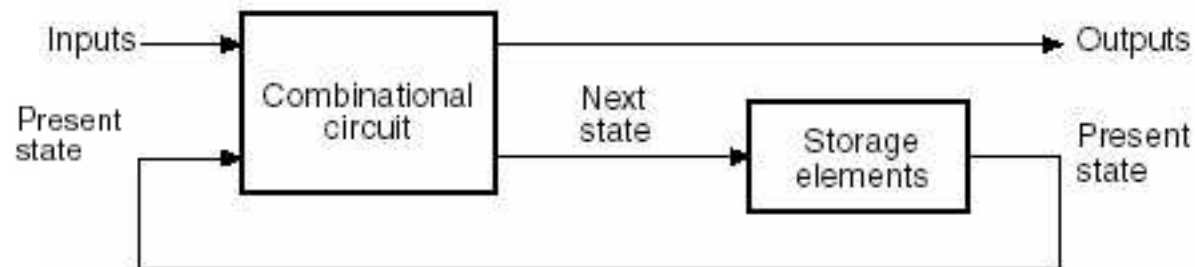


# Example 1: a given FSA

---

 

# Example 1: variables

---

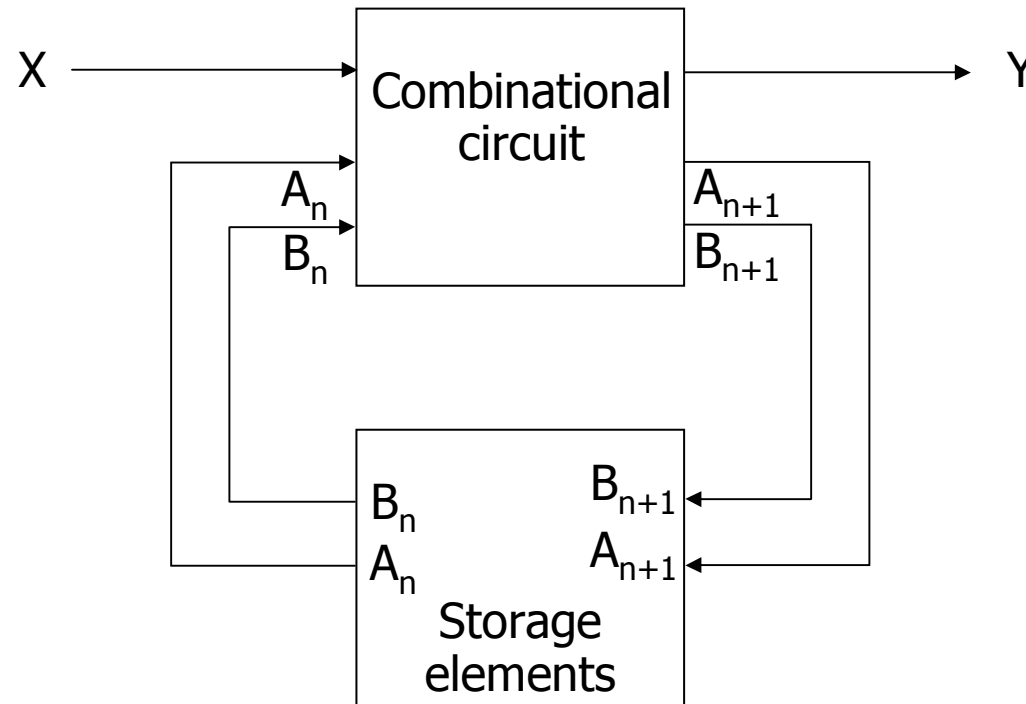

# Example 1: transition tables

---

- Transition table for output and state variables

$A_n$	$B_n$	X	Y	$A_{n+1}$	$B_{n+1}$
0	0	0	0	1	1
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	0	0	1



# Example 1: minimization

State variables

		X	
		0	1
AB	11	1	0
	01	1	0
	00	1	--
	10	0	0

		X	
		0	1
AB	11	0	1
	01	1	0
	00	1	--
	10	1	0

Output

		Y	
		0	1
AB	00	0	--
	01	0	1
	11	1	0
	10	1	1

- NOTE: Unspecified inputs cannot be used for minimization, otherwise a different FSM might be synthesized, i.e. an FSM with more transitions than in the initial specification !

# Example 1: wrong minimization

- Using unspecified inputs for minimization means that we choose value 1 for those we take and 0 for the others ...

		State variables	
		X	
$A_{n+1}$		0	1
AB	11	1	0
	01	1	0
	00	1	--
	10	0	0

		X	
		0	1
$B_{n+1}$		0	1
AB	11	0	1
	01	1	0
	00	1	--
	10	1	0


		Output	
		Y	X
		0	1
AB	00	0	--
	01	0	1
	11	1	0
	10	1	1

... hence we would implement ...
 
# Example 1: the corresponding FSA


---

- ...this FSA which has a different behavior from the original correct one!





 
# Example 1: one more comment...

- By not using unspecified inputs during minimization we are synthesizing this FSA, but this is an acceptable completion of the incompletely specified initial FSA!



# Example 1: circuits

---

 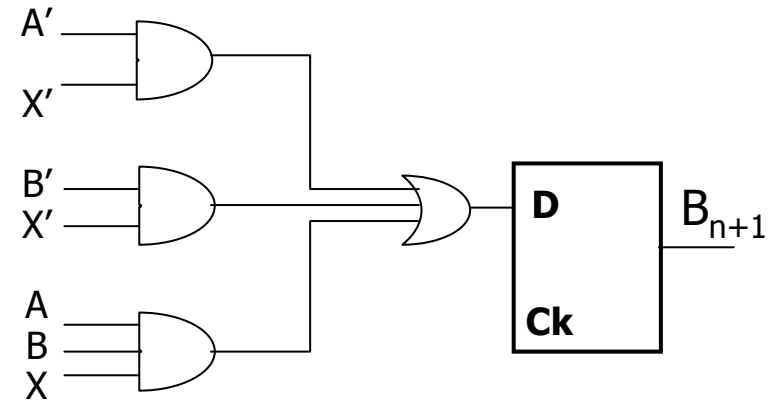 

## Example 2: specification

---


- Two input values are presented together
- Recognize with output 10 and 01, respectively, when a couple 00 or a couple 11 is presented
- Recognize with output 11 when two consecutive couples of identical values are presented
- Example:

INPUT	01	01	00	00	00	11	11	10	11	11	11	11
OUTPUT	00	00	10	11	10	01	11	00	01	11	01	11
 
# Example 2: corresponding FSA


---

- Show also the initial state (double circle)



# Example 2: variables

---

 



# Example 2: transition tables

$A_n$	$B_n$	X	Y	W	Z	$A_{n+1}$	$B_{n+1}$
0	0	0	0	1	0	1	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	1	0	1
0	1	0	0	1	0	1	0
0	1	0	1	0	0	0	0
0	1	1	0	0	0	0	0
0	1	1	1	1	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	0	0	0	0
1	0	1	0	0	0	0	0
1	0	1	1	0	1	0	1
1	1	0	0	--	--	--	--
1	1	0	1	--	--	--	--
1	1	1	0	--	--	--	--
1	1	1	1	--	--	--	--

Rev. 4.1 (2006-07) by Enrico Nardelli

# Example 2: circuits

---

